

-: ASSIGNMENT # 2 SOLUTION :-

Q #1:- Perform the following operations:

a) $2\angle 45^\circ + 3\angle 45^\circ$

Soln-

$2\angle 45^\circ + 3\angle 45^\circ$

First change them in rectangular form.

$2\angle 45^\circ$

, $3\angle 45^\circ$

$x = r \cos \theta = 2 \cos 45^\circ \Rightarrow 1.414$

, $x = r \cos \theta = 3 \cos 45^\circ \Rightarrow 2.121$

$y = r \sin \theta = 2 \sin 45^\circ \Rightarrow 1.414$

, $y = r \sin \theta = 3 \sin 45^\circ \Rightarrow 2.121$

$2\angle 45^\circ \Rightarrow 1.414 + j1.414$

, $3\angle 45^\circ \Rightarrow 2.121 + j2.121$

$$[1.414 + j1.414] + [2.121 + j2.121] = (1.414 + 2.121) + j(1.414 + 2.121) \\ \Rightarrow 3.535 + j3.535.$$



b) $2\angle 0^\circ - 4\angle 180^\circ$

Soln-

First change them in rectangular form.

$2\angle 0^\circ$

, $4\angle 180^\circ$

$x = r \cos \theta = 2 \cos 0^\circ \Rightarrow 2$

, $x = r \cos \theta = 4 \cos 180^\circ \Rightarrow -4$


$y = r \sin \theta = 2 \sin 0^\circ \Rightarrow 0$

, $y = r \sin \theta = 4 \sin 180^\circ \Rightarrow 0$

$2\angle 0^\circ \Rightarrow 2 + j0 \Rightarrow 2$

, $4\angle 180^\circ = -4 + j0 \Rightarrow -4$

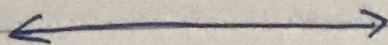$2\angle 0^\circ - 4\angle 180^\circ = 2 - (-4) \Rightarrow 6.$



Date:

$$\frac{C_1}{C_2} = \frac{4.123 \angle 75.9^\circ}{6.403 \angle 51.3^\circ} = \frac{4.123}{6.403} \angle 75.9^\circ - 51.3^\circ$$

$$\frac{C_1}{C_2} \Rightarrow 0.643 \angle 24.6^\circ$$


Question #1
Part C
remaining

Q#28 Find the input voltage e_{in} of the circuit shown below:

$$v_a = 50 \sin(377t + 30^\circ)$$

$$v_b = 30 \sin(377t + 60^\circ)$$

$$f = 60 \text{ Hz}$$

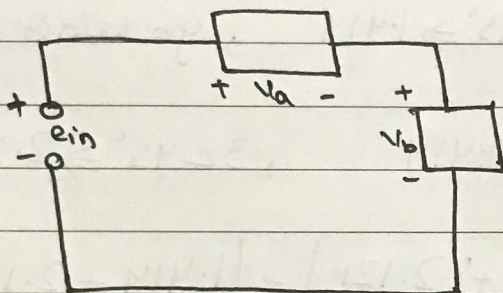

Soln

Applying Kirchhoff's voltage law, we have

$$e_{in} = v_a + v_b$$

Converting from time domain to phasor domain:

$$v_a = 50 \sin(377t + 30^\circ) \text{ V} \Rightarrow \bar{V}_a = 50 \angle 30^\circ$$

$$v_b = 30 \sin(377t + 60^\circ) \text{ V} \Rightarrow \bar{V}_b = 30 \angle 60^\circ$$

Converting in rectangular form:

$$\bar{V}_a = 50 \angle 30^\circ$$

$$\bar{V}_b = 30 \angle 60^\circ$$

$$x = r \cos \theta = 50 \cos 30^\circ \Rightarrow 43.30$$

$$x = r \cos \theta = 30 \cos 60^\circ \Rightarrow 15$$

$$y = r \sin \theta = 50 \sin 30^\circ \Rightarrow 25$$

$$y = r \sin \theta = 30 \sin 60^\circ \Rightarrow 25.98$$

$$\bar{V}_a = (43.30 + j25) \text{ V}$$

$$\bar{V}_b = (15 + j25.98) \text{ V}$$

$$\text{Then, } \bar{E}_{in} = \bar{V}_a + \bar{V}_b$$

$$= (43.30 + j25) + (15 + j25.98)$$

$$= (43.30 + 15) + j(25 + 25.98)$$

$$\bar{E}_{in} \Rightarrow (58.3 \text{ V} + j50.98) \text{ V}$$

Convert \bar{E}_{in} in polar form.

$$r = \sqrt{x^2 + y^2} = \sqrt{(58.3)^2 + (50.98)^2} \Rightarrow 77.44$$

$$\theta = \tan^{-1} \frac{y}{x} = \tan^{-1} \frac{50.98}{58.3} \Rightarrow 41.16^\circ$$


Date:

$$\bar{E}_{in} = 77.44 \angle 41.16^\circ$$

Now convert it in time domain.

$$e_{in} = 77.44 \sin(377t + 41.16^\circ)$$

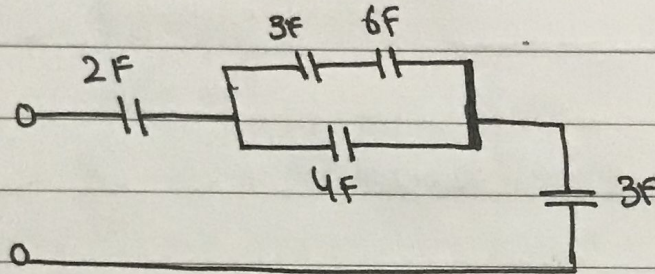Q#3: Determine the equivalent capacitance for the following circuit:




Sol

3F and 6F are in series and parallel with 4.

$$3F \text{ \& \ } 6F \Rightarrow \frac{1}{\frac{1}{3}} + \frac{1}{\frac{1}{6}} = \boxed{2F}$$

~~4F + 3F~~ $4F + 2F \Rightarrow 6F$

Now 2F and 6F and 3F are in series

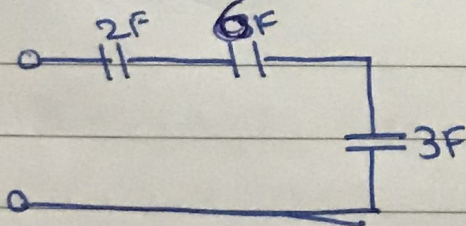

$$\frac{1}{C_T} = \frac{1}{2F} + \frac{1}{6F} + \frac{1}{3F}$$

~~$\frac{1}{C_T} = \frac{1}{2F} + \frac{1}{6F} + \frac{1}{3F}$~~

$$C_T = \frac{1}{\frac{1}{2} + \frac{1}{6} + \frac{1}{3}} \Rightarrow 1F$$

Question #1

Part C

c) $\frac{c_1}{c_2}$ if $c_1 = 1 + j4$ and $c_2 = 4 + j5$

Sol:

First change in polar form.

$$c_1 = 1 + j4$$

$$r = \sqrt{x^2 + y^2} = \sqrt{1^2 + 4^2} \Rightarrow 4.123$$

$$\theta = \tan^{-1} \frac{y}{x} = \tan^{-1} \frac{4}{1} \Rightarrow 75.9^\circ$$

$$c_1 \Rightarrow 4.123 \angle 75.9^\circ$$

$$c_2 = 4 + j5$$

$$r = \sqrt{4^2 + 5^2} \Rightarrow 6.403$$

$$\theta = \tan^{-1} \frac{5}{4} \Rightarrow 51.34^\circ$$

$$c_2 \Rightarrow 6.403 \angle 51.34^\circ$$

PALMATIAN