

LECTURE # 4

1x3

EXAMPLE # 1

- a) Calculate the charge stored on a 3pF capacitor with 20V across it.

Sol:

$$q = Cv$$

$$q = 3 \times 10^{-12} \times 20 \Rightarrow 60 \text{ pC}$$

- b) Find the energy stored in the capacitor.

Sol:

The energy stored is :

$$w = \frac{1}{2} Cv^2$$

$$= \frac{1}{2} \times (3 \times 10^{-12}) \times (20)^2$$

$$w = \frac{1}{2} \times 3 \times 10^{-12} \times 400 \Rightarrow 600 \text{ pJ}$$

EXAMPLE # 2

The voltage across a 5-μF capacitor is :

$$v(t) = 10 \cos(6000t) \text{ V}$$

Calculate the current through it.

Sol:

By definition, the current is


$$i(t) = C \frac{dv}{dt} = 5 \times 10^{-6} \frac{d}{dt} (10 \cos 6000t)$$

$$= -5 \times 10^{-6} \times 10 \sin 6000t \times 6000$$


$$i(t) \Rightarrow -0.3 \sin 6000t$$

EXAMPLE # 38-

Obtain the energy stored in the capacitor shown below under the dc conditions:-

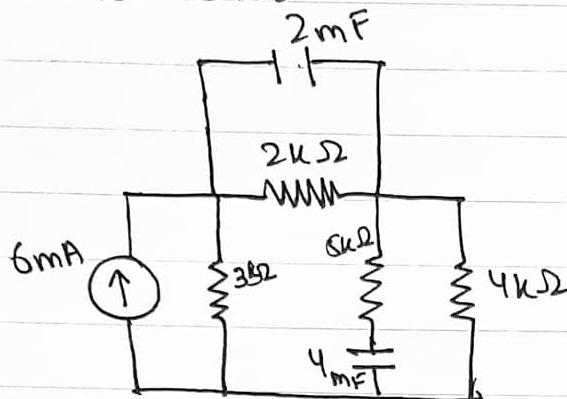Sol:

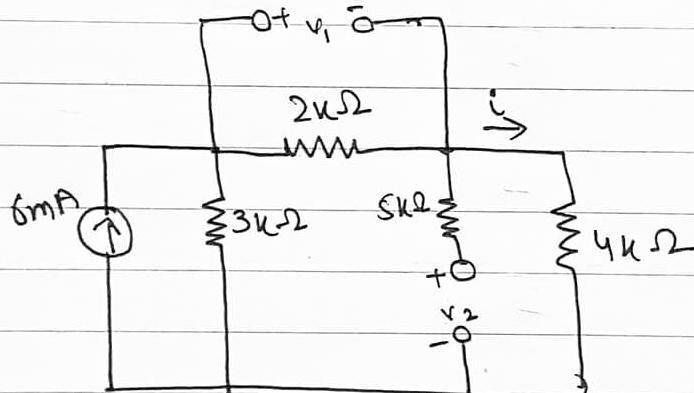Under dc conditions, we replace each capacitor with an open circuit, as shown below:-



The current through the series combination of the $2\text{k}\Omega$ and $4\text{k}\Omega$ resistors is obtained by current division as:

$$\begin{aligned} i &= \frac{3}{3+2+4} (6\text{mA}) \\ &= \frac{3}{9} (6^2 \text{mA}) \Rightarrow 2\text{mA} \end{aligned}$$

Hence, the voltages v_1 and v_2 across the capacitors are:

$$v_1 = 2000i \Rightarrow 4V$$

$$v_2 = 4000i = 4000(2mA) \Rightarrow 8V$$


and the energies stored in them are:

$$w_1 = \frac{1}{2} C_1 v_1^2 = \frac{1}{2} (2 \times 10^{-3}) (4)^2 \Rightarrow 16mJ$$

$$w_2 = \frac{1}{2} C_2 v_2^2 = \frac{1}{2} (4 \times 10^{-3}) (8)^2 \Rightarrow 128mJ$$

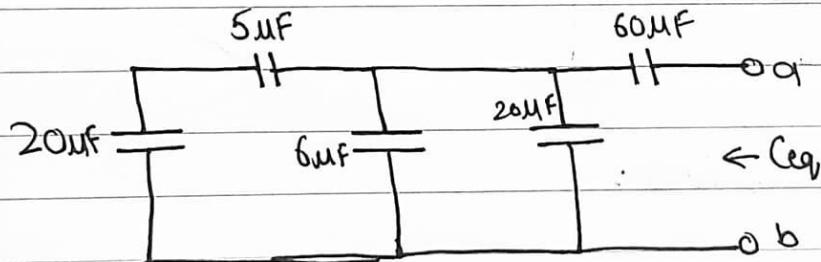EXAMPLE #4:-

Find the equivalent capacitance seen between terminals a and b of the circuit shown below:-



SOL

The $20\mu F$ and $5\mu F$ capacitors are in series; their equivalent capacitance is :

$$\frac{20 \times 5}{20 + 5} = 4\mu F$$

$$\therefore \frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} \text{ for series}$$

Day/Date

This $4\mu F$ capacitor is in parallel with the $6\mu F$ and $20\mu F$ capacitors; their combined capacitance is:


$$4 + 6 + 20 = 30\mu F \quad \therefore C_{eq} = C_1 + C_2 + \dots + C_n \text{ for parallel}$$

This $30\mu F$ capacitor is in series with the $60\mu F$ capacitor. Hence, the equivalent capacitance for the entire circuit is:

$$C_{eq} = \frac{30 \times 60}{30 + 60} \Rightarrow 20\mu F$$

Example #5:-

Consider the circuit shown below

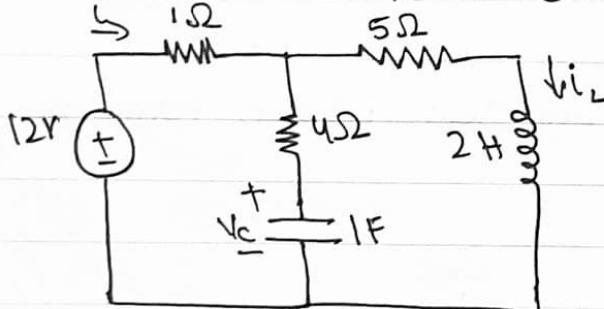


a) Under dc conditions, find:

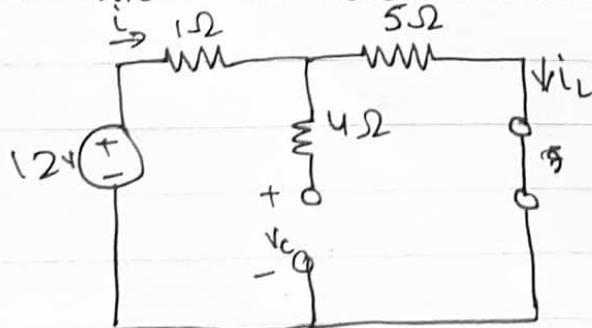a) i , v_c and i_L .

Sol:-

Under dc conditions, we replace the capacitor with an open circuit and the inductor with a short circuit as shown below:



$$i = i_L = \frac{12}{1+5} \Rightarrow 2A$$

The voltage V_C is the same as the voltage across 5Ω resistor. Hence,

$$V_C = 5i = 5 \times 2 \Rightarrow 10V$$

b) the energy stored in the capacitor and inductor.

Sols:-

The energy stored in the capacitor is :


$$\begin{aligned} W_C &= \frac{1}{2} C V_C^2 \\ &= \frac{1}{2} (1) (10)^2 \Rightarrow 50J \end{aligned}$$

and that in the inductor is :-

$$W_L = \frac{1}{2} L i_L^2 = \frac{1}{2} (2)(2^2) \Rightarrow 4J$$

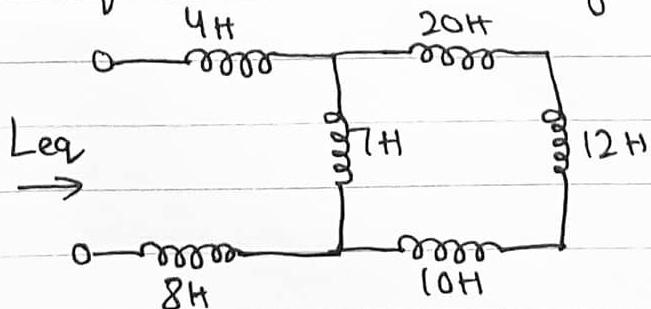EXAMPLE # 6 :-

Find the equivalent inductance of the circuit shown below



Sols:-

The 10H, 12H and 20H inductors are in series; thus, combining them gives a ~~20H~~ 42H inductance.

The 42 H inductor is in parallel with the 7 H inductor so that they are combined, to give

$$\frac{7 \times 42}{7+42} \Rightarrow 6\text{H}$$

This 6H inductor is in series with the 4-H and 8-H inductors. Hence,

$$L_{eq} = 4 + 6 + 8 \Rightarrow 18\text{H}$$