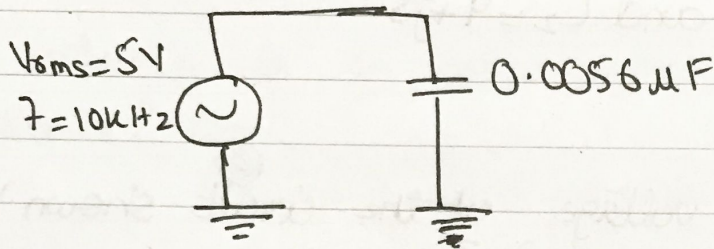


Day/Date MONDAY / 23-4-18

LECTURE #5:-

EXAMPLE #1:-

Determine the rms current:-



Soln-

First, determine the capacitive reactance:-


$$X_C = \frac{1}{2\pi fC} = \frac{1}{2\pi(10 \times 10^3)(0.0056 \times 10^{-6})} \Rightarrow 2.84 k\Omega$$

Then apply Ohm's law:-

$$I_{rms} = \frac{V_{rms}}{X_C} \Rightarrow \frac{5V}{2.84 k\Omega} \Rightarrow 1.76 mA$$

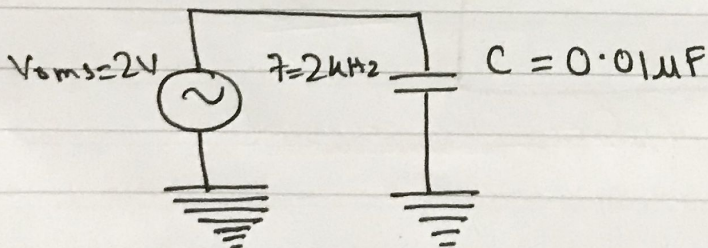EXAMPLE #2:-

Determine the true power and the reactive power:-



Soln-


The true power P_{true} , is always zero for an ideal capacitor. The reactive power is determined by first finding the value of the capacitive reactance and then using $P_o = \frac{V_{rms}^2}{X_C}$.

$$X_C = \frac{1}{2\pi fC} = \frac{1}{2\pi(2 \times 10^3)(0.01 \times 10^{-6})} \Rightarrow 7.96 \text{ k}\Omega$$

$$P_s = \frac{V_{\text{rms}}^2}{X_C} = \frac{(2\text{V})^2}{7.96 \times 10^3} \Rightarrow 503 \mu\text{VAR}$$

EXAMPLE #3:-

Determine the rms current in figure belows

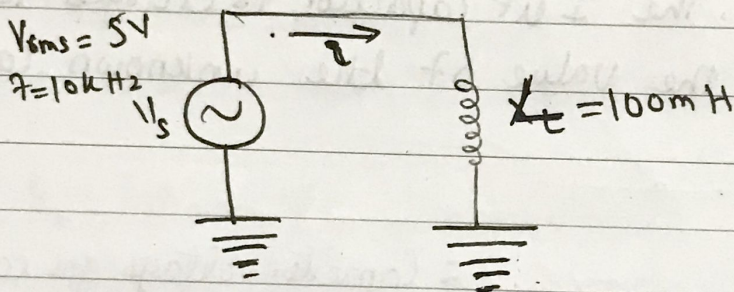Soln

$$X_L = 2\pi fL = 2\pi \times (10 \times 10^3) \times (100 \times 10^{-3})$$

$$\Rightarrow 6283 \Omega$$

To determine rms current apply Ohm's law,

$$I_{\text{rms}} = \frac{V_{\text{rms}}}{X_L} \Rightarrow \frac{5\text{V}}{6283} \Rightarrow 796 \mu\text{A}$$

EXAMPLE #4:-

A 10Vrms signal with a frequency of 1kHz is applied to a 10mH coil with a negligible winding resistance. Determine the reactive power?

Soln

First, calculate the inductive reactance and current values.

$$X_L = 2\pi fL = 2\pi(1 \times 10^3)(10 \times 10^{-3}) \Rightarrow 62.8 \Omega$$

$$I = \frac{V_s}{X_L} = \frac{10}{62.8} \Rightarrow 159 \text{ mA}$$

Then,

$$P_c = I^2 \times R = (159 \text{ mA})^2 (62.8 \Omega) \Rightarrow 1.59 \text{ VAR}$$

EXERCISE PROBLEMS

Problem # 18

Two series capacitors (one $1 \mu\text{F}$, the other of unknown value) are charged from a 12V source. The $1 \mu\text{F}$ capacitor is charged to 8V and the other to 4V . What is the value of the unknown capacitor?

Soln

$$V_T = 12\text{V}$$

$$V_1 = \left(\frac{C_T}{C_1} \right) V_T$$

\therefore Capacitor voltage for capacitor in series

$$8\text{V} = \left(\frac{C_T}{1 \times 10^{-6}} \right) 12\text{V}$$

$$C_T = \left(\frac{8\text{V}}{12\text{V}} \right) 1 \times 10^{-6} \Rightarrow 0.666 \mu\text{F}$$

$$V_2 = \left(\frac{C_T}{C_2} \right) V_T$$

$$C_2 = \frac{C_T V_T}{V_2}$$

$$= \frac{0.66 \times 10^{-6} \times 12\text{V}}{4\text{V}} \Rightarrow 2 \mu\text{F}$$

PROBLEM #2a

A sinusoidal voltage of 20V_{rms} produces an rms current of 100mA when connected to a certain capacitor. What is the reactance?

Sol:

$$X_C = ?$$

$$V_{\text{rms}} = 20\text{V}_{\text{rms}}$$

$$I_{\text{rms}} = 100\text{mA}$$


$$P_0 = V_{\text{rms}} I_{\text{rms}} \\ = 20 \times 100 \times 10^{-3} \Rightarrow 2\text{VAR}$$

$$P_0 = I_{\text{rms}}^2 X_C$$

$$X_C = \frac{P_0}{I_{\text{rms}}^2} = \frac{2\text{VAR}}{(100 \times 10^{-3})^2} \Rightarrow 200\ \Omega$$


PROBLEM #3a-

Determine the total inductance of each circuit shown below

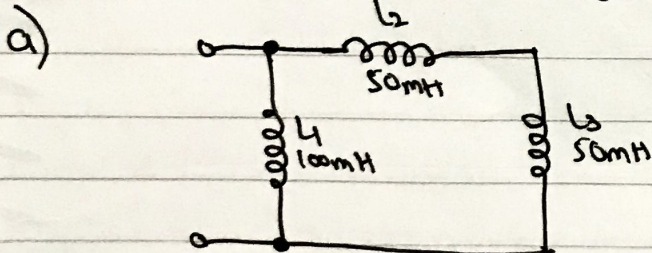Sol:

L_2 and L_3 are in series
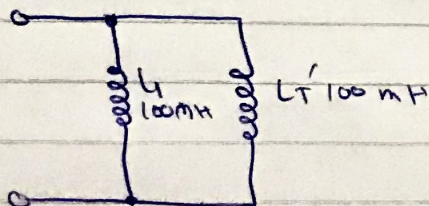
$$L' = L_2 + L_3 \Rightarrow 50\text{mH} + 50\text{mH} \Rightarrow 100\text{mH}$$




Day/Date

Now, L_T' and L_4 are in parallel.

$$L_T = \frac{1}{\frac{1}{L_T'} + \frac{1}{L_4}} = \frac{1}{\frac{1}{100} + \frac{1}{100}} \Rightarrow 50 \text{ mH}$$

b)

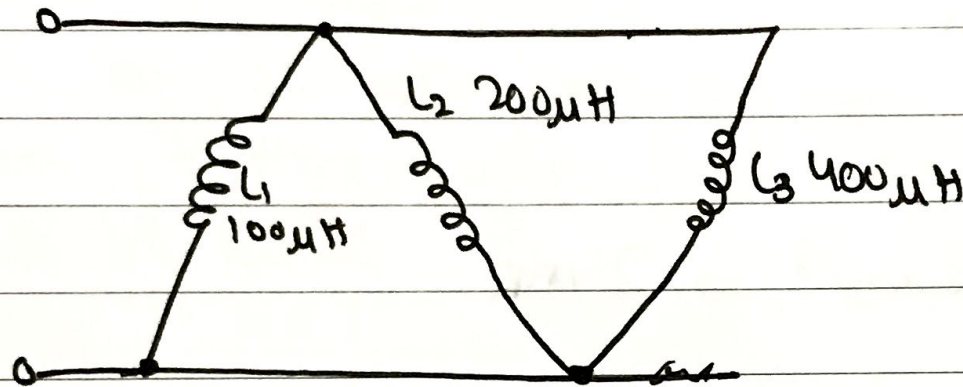

Soln-

all are in parallel, hence:-

$$L_T = \frac{1}{\frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3}} = \frac{1}{\frac{1}{100} + \frac{1}{200} + \frac{1}{400}} \Rightarrow 57.1 \mu\text{H}$$