



# ISRA UNIVERSITY

Islamabad Campus

**B.TECH (Electrical)  
Semester – Spring 2018**

**ETCA-252 Circuit Analysis-2**

**Quiz – 2**

**Marks: 10**


**Handout Date: 23/04/2018**

**Question # 1:**

Given  $Z_1 = 8\angle -30^\circ$  and  $Z_2 = 2\angle -60^\circ$ . Find  $\frac{Z_1}{Z_2}$  and express the result in rectangular form.

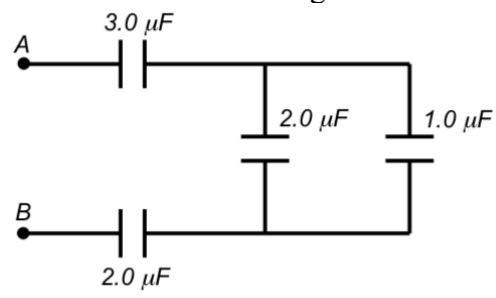**Question # 2:**

Calculate the total capacitance of the following circuit:



**Good Luck**