



ISRA UNIVERSITY

Islamabad Campus

Program: BTECH (Electrical)
Semester – Spring 2018

ETCA-252 Circuit Analysis-II

Assignment – 4 & 5
Marks: 50

Due Date: 19/06/2018
Handout Date: 29/05/2018

Question # 1:

Perform the following operations:


1. $(8 + j5) + (2 + j1)$
2. $(3 + j4) - (1 + j2)$
3. *Multiply:* $(50\angle 10^\circ)(30\angle -60^\circ)$

(Marks 06)

Question # 2:

For the circuit in figure below, determine the following in polar form:


1. Z
2. I_{tot}
3. V_R
4. V_C

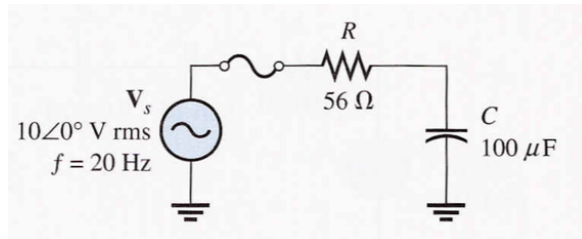

(Marks 10)

Question # 3:


Determine the magnitude and phase angle of the total impedance:

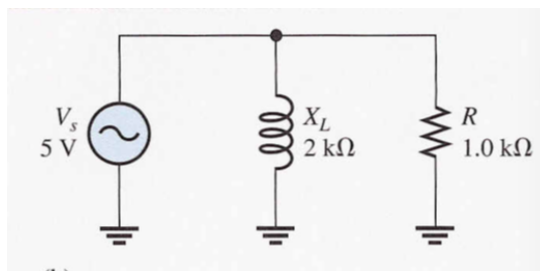

(Marks 10)

Question # 4:


Find the total current in the load resistor, R_L . Assume the sources are ideal.

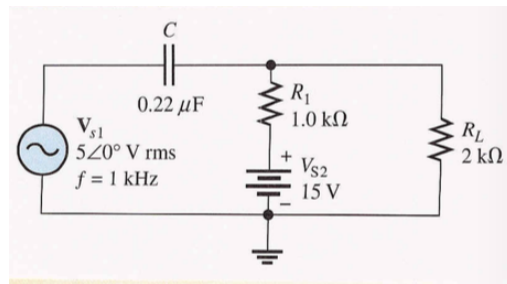

(Marks 10)

Question # 5:


Determine V_{th} and Z_{th} for the circuit within the beige box and draw its Thevenin Equivalent.

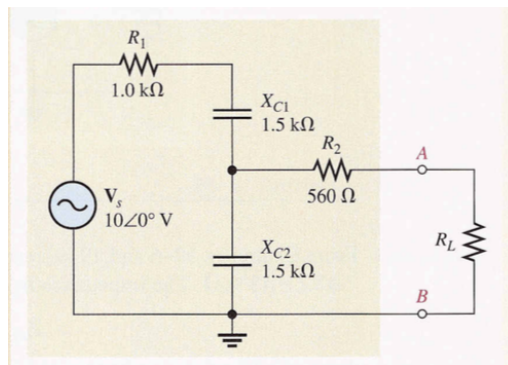

(Marks 10)

Question # 6:

For a given circuit, $I_n = 5\angle 0^\circ mA$, and $Z_n = 150 \Omega + j100\Omega$. Draw the Norton equivalent circuit.

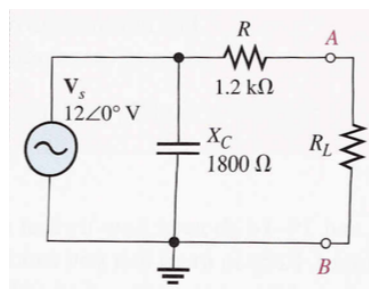

(Marks 04)

Good Luck