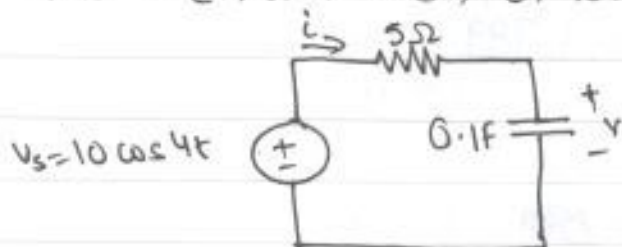


→ LECTURE # 7 →

EXAMPLE # 1:-Find $v(t)$ and $i(t)$ in the circuit shown below:SolnFrom the voltage source, $\bar{V}_s = 10 \angle 0^\circ \text{ V}$

The impedance is:

$$\begin{aligned}\bar{Z} &= 5 + \frac{1}{j\omega C} = 5 + \frac{1}{j4 \times 0.1} \\ &= 5 - j2.5 \Omega\end{aligned}$$

Hence the current

$$\bar{I} = \frac{\bar{V}_s}{\bar{Z}} = \frac{10 \angle 0^\circ}{5 - j2.5 \Omega}$$

 $\bar{Z} = 5 - j2.5 \Omega$ convert in polar form

$$\begin{aligned}|Z| &= \sqrt{R^2 + X^2} & , \theta &= \tan^{-1} \frac{X}{R} \\ &= \sqrt{5^2 + (-2.5)^2} \Rightarrow 5.59 & , &= \tan^{-1} \frac{-2.5}{5} = -26.5^\circ\end{aligned}$$

$$\begin{aligned}\bar{I} &= \frac{\bar{V}_s}{\bar{Z}} = \frac{10 \angle 0^\circ}{5.6 \angle -26.5^\circ} \\ &= \frac{10}{5.6} \angle 0^\circ - (-26.5^\circ)\end{aligned}$$

$$\bar{I} = 1.78 \angle 26.5^\circ$$

The voltage across the capacitor is :

$$\begin{aligned}\bar{V} &= \bar{I} Z_c \\ &= \frac{\bar{I}}{j\omega C} = \frac{1.789 \angle 26.57^\circ}{j4 \times 0.1} \\ &= 1.789 \angle 26.57^\circ\end{aligned}$$

$$j0.4 \Rightarrow |Z| = \sqrt{(0)^2 + (0.4)^2} \Rightarrow 0.4$$

~~Phase angle~~ $\theta = 90^\circ$

$$\begin{aligned}\bar{V} &= \frac{1.789 \angle 26.57^\circ}{0.4 \angle 90^\circ} \\ &= \frac{1.789}{0.4} \angle 26.57^\circ - 90^\circ \Rightarrow 4.47 \angle -63.43^\circ\end{aligned}$$


Converting \bar{I} and \bar{V} to the time domain, we get

$$i(t) = 1.789 \cos(4t + 26.57^\circ) \text{ A}$$

$$v(t) = 4.47 \cos(4t - 63.43^\circ) \text{ V}$$

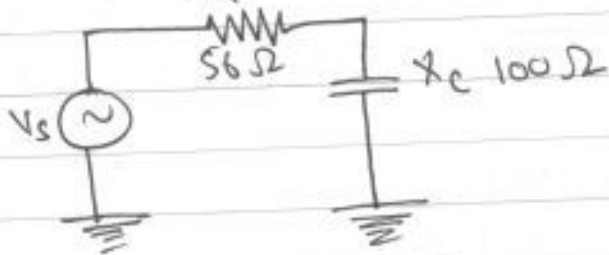EXAMPLE # 20-

For the circuit below write the phasor expression for the impedance in both rectangular and polar form.:-



Sol:-

$$\begin{aligned}Z &= R - jX_c \quad \text{in Rectangular form} \\ &= 56 - j100 \Omega\end{aligned}$$

The impedance in polar form is :-

$$|Z| = \sqrt{R^2 + X_c^2}$$

$$= \sqrt{(56)^2 + (+100)^2}$$

$$|Z| \Rightarrow 114.6 \approx 115$$

$$\theta = \tan^{-1}\left(\frac{X_c}{R}\right)$$


$$\theta = \tan^{-1}\left(\frac{-100}{56}\right) \Rightarrow -60.8^\circ$$

$$\bar{Z} = |Z| \angle \theta$$

$$= 115 \angle -60.8^\circ \Omega$$

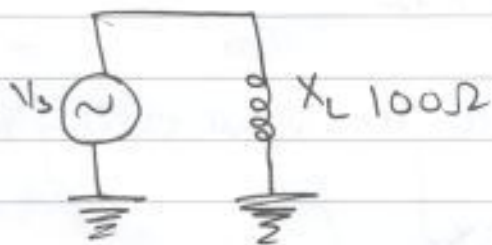EXAMPLE # 3:-

For the circuit below write the phasor expression for the impedance in both rectangular and polar form:



Sols:-

The impedance in rectangular form is

$$Z = 0 + jX_L \Rightarrow j100 \Omega \quad \text{as } R=0$$

The impedance in polar form is :-


$$|Z| = \sqrt{0^2 + 100^2} \Rightarrow 100$$

$$\theta = 90^\circ$$

$$Z = 100 \angle 90^\circ \Omega$$

EXAMPLE #4

Determine the current in the circuit shown below, and draw a phasor diagram showing the relation b/w source voltage and current.

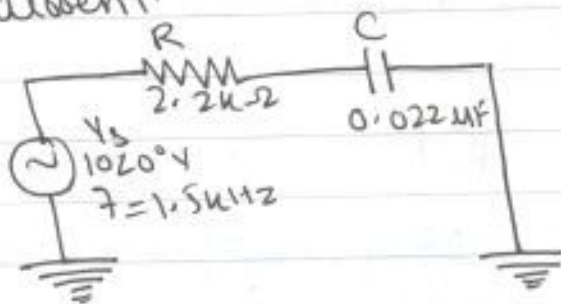Soln

The magnitude of the capacitive reactance is,

$$X_c = \frac{1}{2\pi f C}$$

$$= \frac{1}{2\pi (1.5 \text{ kHz}) (0.022 \times 10^{-6})}$$

$$X_c = 4.82 \text{ k}\Omega$$

The total impedance in rectangular form is,

$$Z = R - jX_c$$

$$= 2.2 \text{ k}\Omega - j4.82 \text{ k}\Omega$$

Converting Z in polar form.

$$|Z| = \sqrt{R^2 + X_c^2}$$

$$= \sqrt{(2.2 \text{ k})^2 + (4.82 \text{ k})^2}$$

$$|Z| \Rightarrow 5.30 \text{ k}$$

$$\theta = \tan^{-1} \frac{X_c}{R}$$

$$= \tan^{-1} \frac{4.82 \text{ k}}{2.2 \text{ k}}$$

$$\theta \Rightarrow -65.5^\circ$$


$$Z = 5.30 \angle -65.5 \text{ k}\Omega$$

Use Ohm's law to determine the current

$$\begin{aligned}\bar{I} &= \frac{\bar{V}}{Z} = \frac{10 \angle 0^\circ \text{ V}}{5.30 \angle -65.5^\circ \text{ k}\Omega} \\ &= \frac{10}{5.30} \angle 0 - (-65.5)\end{aligned}$$


$$\bar{I} = 1.89 \angle 65.5^\circ \text{ mA}$$

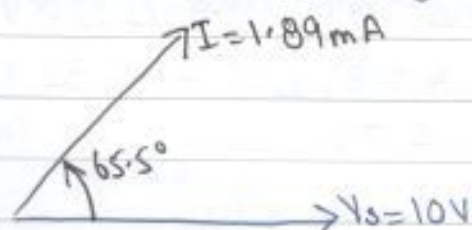The magnitude of the current is 1.89 mA. The positive phase angle of 65.5° indicates that the current leads the voltage by that amount, as shown in the phasor diagram below:



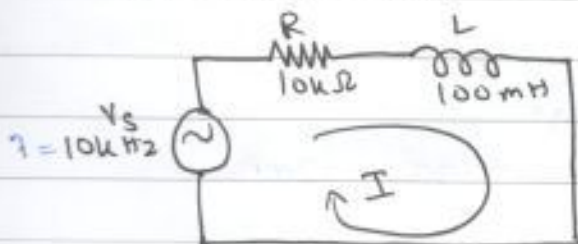EXAMPLE #5:

$$\bar{I} = 0.2 \angle 0^\circ \text{ mA}$$



Soln

The magnitude of the inductive reactance is:

$$\begin{aligned}X_L &= 2\pi fL \\ &= 2\pi (10 \times 10^3) (100 \times 10^{-3}) \Rightarrow 6.28 \text{ k}\Omega\end{aligned}$$

The impedance in rectangular form is

$$\begin{aligned}Z &= R + jX_L \\ &= 10 \text{ k}\Omega + j6.28 \text{ k}\Omega\end{aligned}$$

Converting to polar fields

$$Z = \sqrt{R^2 + X_L^2} \angle \tan^{-1} \left(\frac{X_L}{R} \right)$$

$$= \sqrt{10k^2 + (6.28k)^2} \angle \tan^{-1} \left(\frac{6.28}{10} \right)$$

$$Z \Rightarrow 11.8 \angle 32.1^\circ k\Omega$$

Use Ohm's law to determine the source voltage.


$$V_s = \bar{I} Z$$

$$= (0.2 \angle 0^\circ \text{ mA}) (11.8 \angle 32.1^\circ k\Omega)$$

$$= (0.2 \times 11.8) \angle 0^\circ \text{ mA} + 32.1^\circ k\Omega$$


$$V_s = 2.36 \angle 32.1^\circ \text{ V}$$

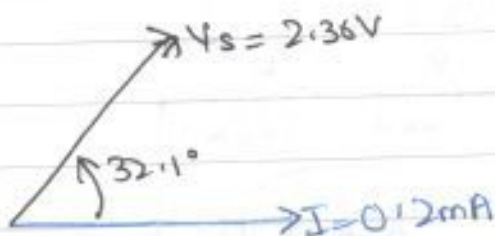The magnitude of the source voltage is 2.36V at an angle of 32.1° with respect to the current. The voltage leads the current by 32.1° .



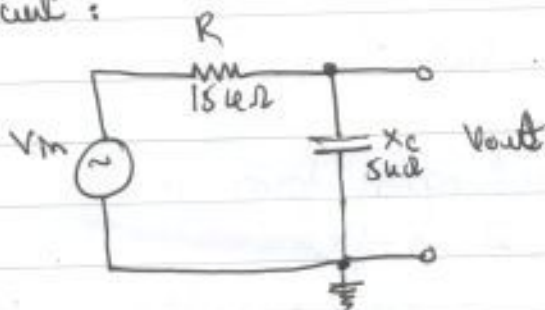EXAMPLE #6:-

Determine the amount of ^{phase} lag from input to output in following lag circuit:



Soln


For the lag circuit

$$\phi = -\tan^{-1} \left(\frac{R}{X_c} \right) = -\tan^{-1} \left(\frac{15k\Omega}{5k\Omega} \right)$$

$$\phi = -71.6^\circ$$

The output lags the input by 71.6° .EXAMPLE #7

Calculate the o/p phase angle for the following circuit:

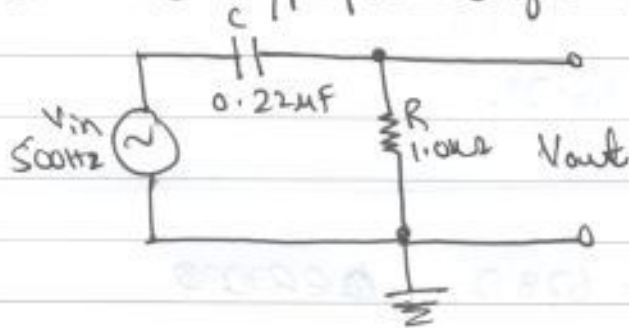Soln


First determine the capacitive reactance.

$$X_c = \frac{1}{2\pi f C}$$

$$= \frac{1}{2\pi (500\text{Hz})(0.22 \times 10^{-6})} \Rightarrow 1.45k\Omega$$

$$\phi = \tan^{-1} \left(\frac{X_c}{R} \right) = \tan^{-1} \left(\frac{1.45k\Omega}{1.0k\Omega} \right) \Rightarrow 55.4^\circ$$

The o/p leads by 55.4° .

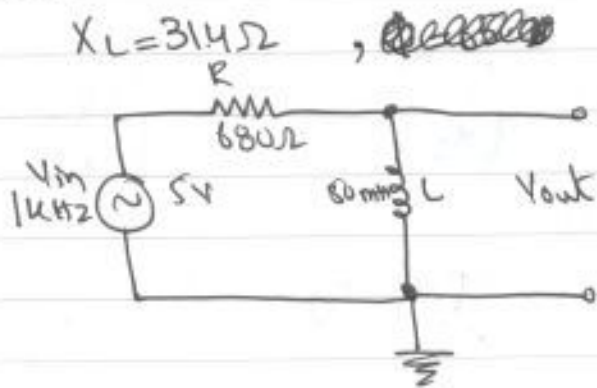
EXAMPLE #8:-Soln-

$$\phi = \tan^{-1} \left(\frac{R}{X_L} \right) = \tan^{-1} \left(\frac{680 \Omega}{314 \Omega} \right) \Rightarrow 65.2^\circ$$

The o/p leads the i/p by 65.2° .

EXAMPLE #9:-

$V = 10V$, $X_L = 628 \Omega$, ~~$X_L = 628 \Omega$~~

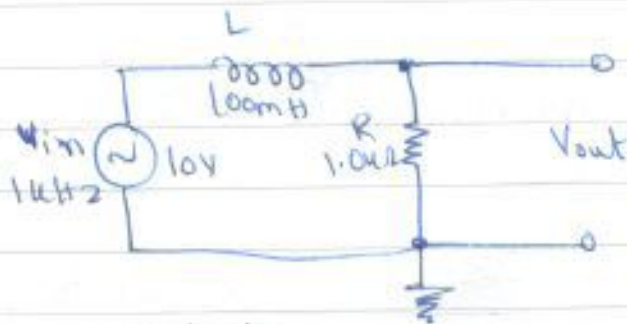Soln-

$$\begin{aligned} \phi &= -\tan^{-1} \left(\frac{X_L}{R} \right) \\ &= -\tan^{-1} \left(\frac{628 \Omega}{1 \text{ k}\Omega} \right) \Rightarrow -32.1^\circ \end{aligned}$$

The o/p lags the input by 32.1° .