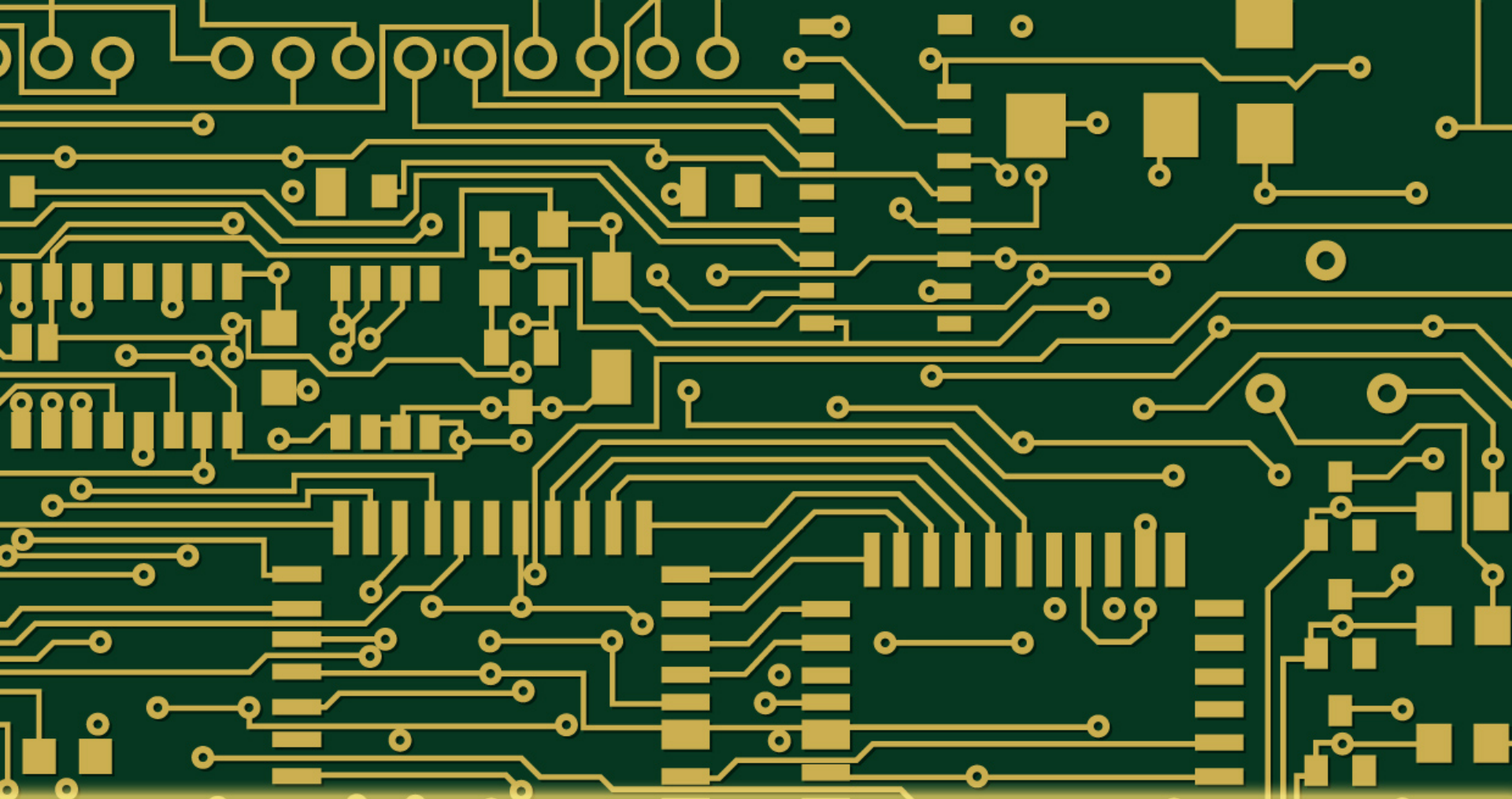


# Circuit Analysis-II



# Impedance & Admittance

# Impedance

- ✓ The voltage-current relations for the three passive elements are:

$$\bar{V} = R\bar{I}, \quad \bar{V} = j\omega L\bar{I}, \quad \bar{V} = \frac{\bar{I}}{j\omega C}$$

- ✓ These equations may be written in terms of the ratio of the phasor voltage to the phasor current as:

$$\frac{\bar{V}}{\bar{I}} = R, \quad \frac{\bar{V}}{\bar{I}} = j\omega L, \quad \frac{\bar{V}}{\bar{I}} = \frac{1}{j\omega C}$$

- ✓ From these three expressions we obtain Ohm's law in phasor form for any type of element:

$$Z = \frac{\bar{V}}{\bar{I}} \quad \text{or} \quad \bar{V} = Z\bar{I}$$

# Impedance (cont.)

- ✓ Where  $Z$  is a frequency-dependent quantity known as impedance, measured in ohms.
- ✓ The impedance  $Z$  of a circuit is the ratio of the phasor voltage  $\mathbf{V}$  to the phasor current  $\mathbf{I}$ , measured in ohms  $\Omega$ .
- ✓ The impedance represents the opposition that the circuit exhibits to the flow of sinusoidal current.
- ✓ The impedance is the ratio of two Phasors, but it is not a phasor because it does not correspond to a sinusoidal varying quantity.
- ✓ Consider two extreme cases of angular frequency:
  - ✓ When  $\omega=0$   $Z_L=0$  and  $Z_C \rightarrow \infty$  confirming that inductor act as a short circuit while capacitor acts like an open circuit.
  - ✓ When  $\omega \rightarrow \infty$   $Z_L \rightarrow \infty$  and  $Z_C=0$ , indicates that the inductor is an open circuit while capacitor is a short circuit.

# Impedance (cont.)

- ✓ As a complex quantity impedance can be expressed as:

$$Z = R + jX$$

$$Z = |Z| \angle \theta$$

$$\text{where } |Z| = \sqrt{R^2 + X^2}, \quad \theta = \tan^{-1} \frac{X}{R}$$

$$\text{and } R = |Z| \cos \theta, \quad X = |Z| \sin \theta$$

- ✓ Where  $R = \text{Re } Z$  is the resistance and  $X = \text{Im } Z$  is the reactance.
- ✓ The reactance  $X$  may be positive or negative.
- ✓ The impedance is inductive when  $X$  is positive or capacitive when  $X$  is negative.
- ✓ Thus, impedance  $Z = R + jX$  is said to be inductive or lagging since current lags voltage.

# Impedance (cont.)

- ✓ While impedance  $Z=R-jX$  is capacitive or leading because current leads voltage.
- ✓ Impedances and admittances of passive elements:

<b>Element</b>	<b>Impedance</b>	<b>Admittance</b>
$R$	$Z = R$	$Y = \frac{1}{R}$
$L$	$Z = j\omega L$	$Y = \frac{1}{j\omega L}$
$C$	$Z = \frac{1}{j\omega C}$	$Y = j\omega C$


# Admittance

- ✓ The admittance  $Y$  is the reciprocal of impedance, measured in siemens (S).
- ✓ The admittance  $Y$  of an element is the ratio of the phasor current through it to the phasor voltage across it:

$$Y = \frac{1}{Z} = \frac{\bar{I}}{\bar{V}}$$
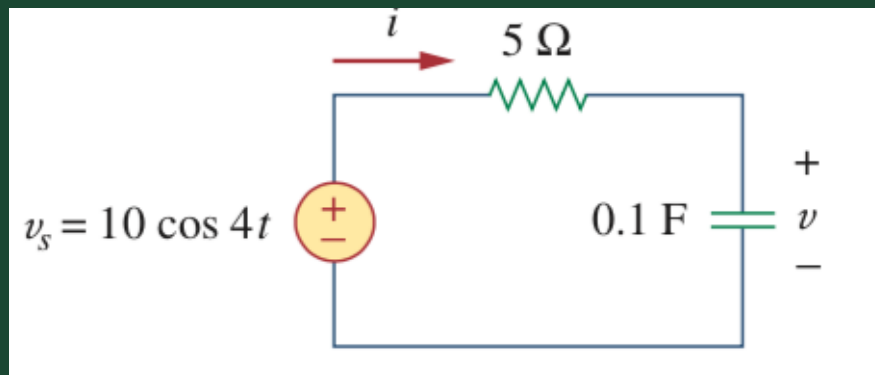
# Example #1


- ✓ Find  $v(t)$  and  $i(t)$  in the circuit shown below:





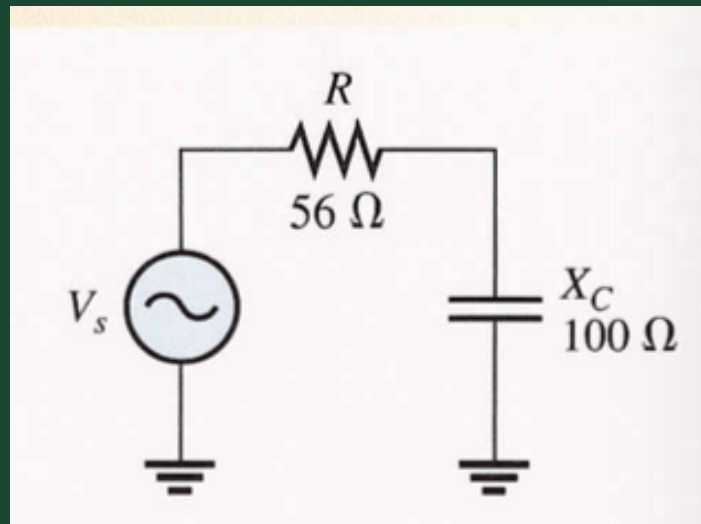
# Example #2


- ✓ For the circuit below write the phasor expression for the impedance in both rectangular and polar form:


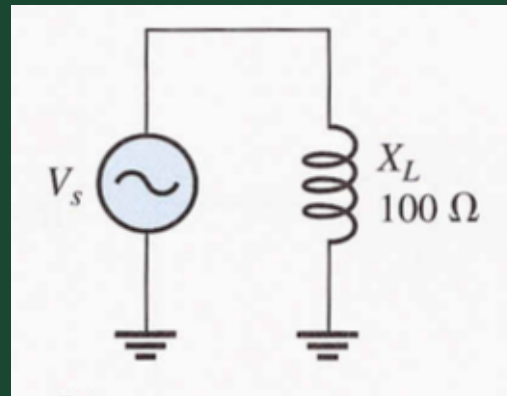
# Example #3

- ✓ For the circuit below write the phasor expression for the impedance in both rectangular and polar form:



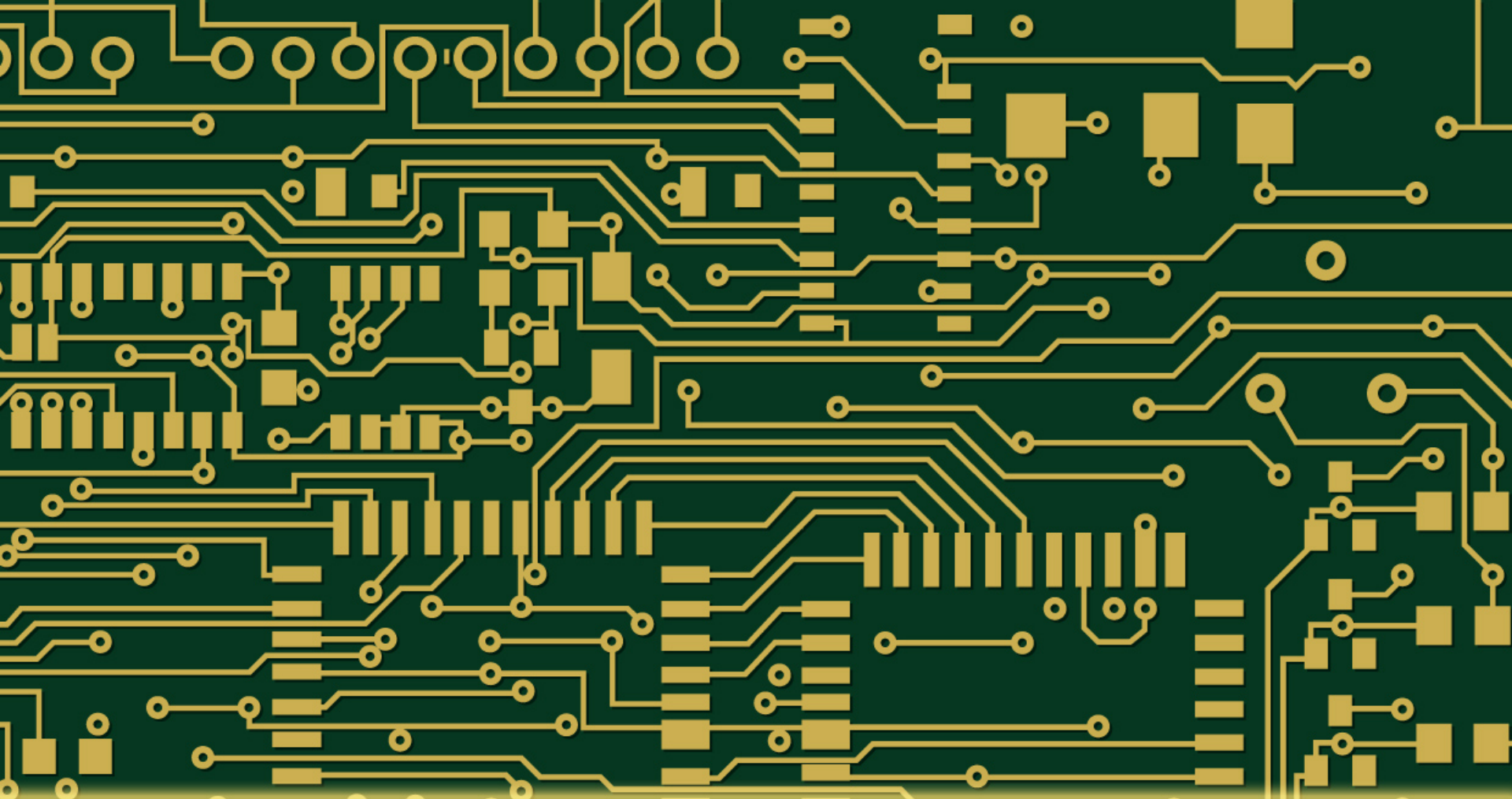

# Analysis of Series Circuits


# Series RC & RL Circuits

- ✓ For the analysis of series RC circuits Ohm's law can be used, which involves the phasor quantities of  $\mathbf{Z}$ ,  $\mathbf{V}$ , and  $\mathbf{I}$ .
- ✓ The three equivalent forms of Ohm's law are as follows:

$$\bar{V} = \bar{I}Z, \quad \bar{I} = \frac{\bar{V}}{Z}, \quad Z = \frac{\bar{V}}{\bar{I}}$$

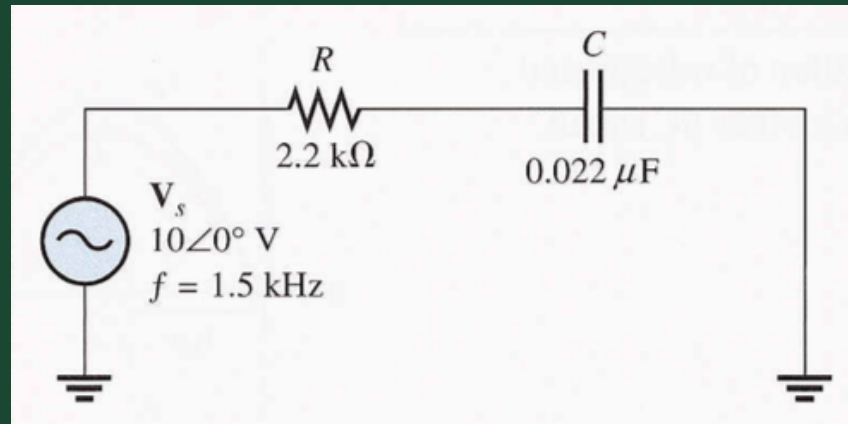
# Example #4


- ✓ Determine the current in the circuit shown below, and draw a phasor diagram showing the relation between source voltage and current.


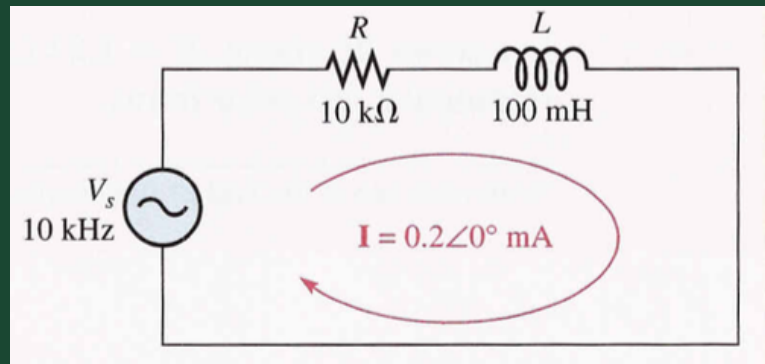
# Example #5

- ✓ The current in figure below is expressed in polar form as  $\bar{I} = 0.2\angle 0^\circ \text{ mA}$ . Determine the source voltage expressed in polar form, and draw a phasor diagram showing relationship between the source voltage and the current.




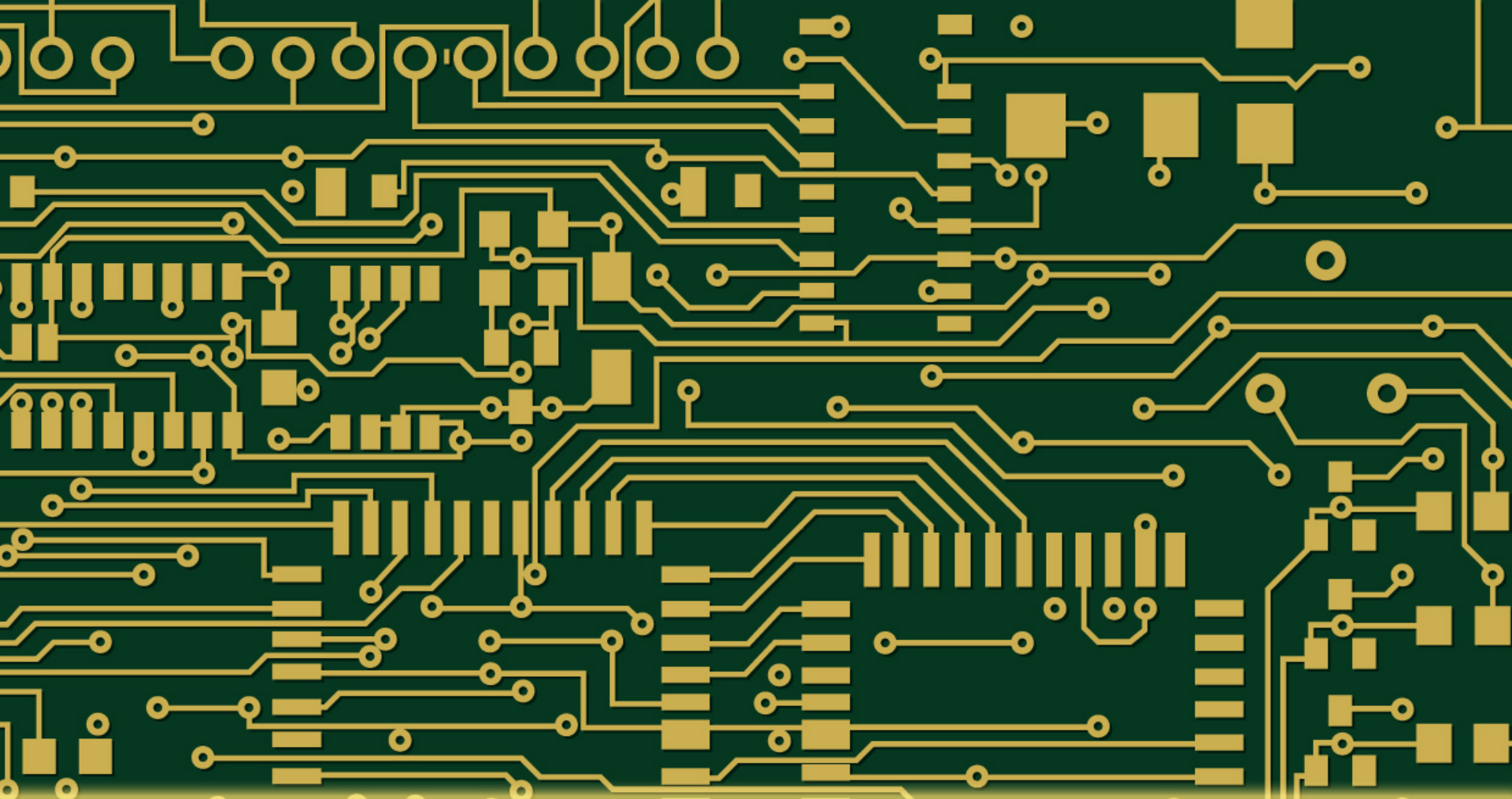

# Phase Relationships of Current & Voltages
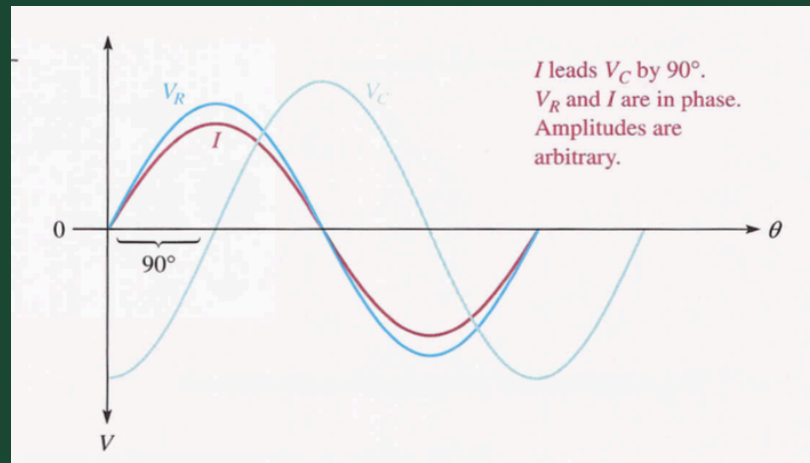
# Series RC Circuit


- ✓ In a series RC circuit, the current is the same through both the resistor and capacitor.
- ✓ Thus, the resistor voltage is in phase with the current and the capacitor voltage lags the current by  $90^\circ$ .
- ✓ Therefore, there is a phase difference of  $90^\circ$  between the resistor voltage,  $V_R$  and the capacitor voltage  $V_C$ .





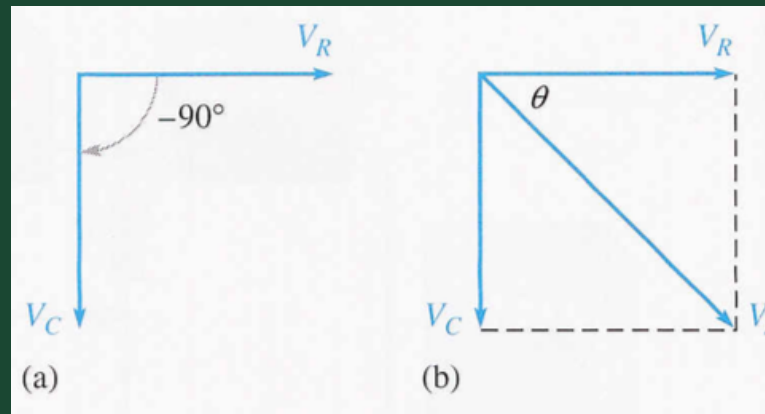
# Series RC Circuit (cont.)


- ✓ From Kirchhoff's voltage law, the sum of the voltage drops must equal the applied voltage.
- ✓ Since  $V_R$  and  $V_C$  are not in phase with each other they must be added as phasor quantities.
- ✓ Voltage phasor diagram for a series RC circuit is as follows:


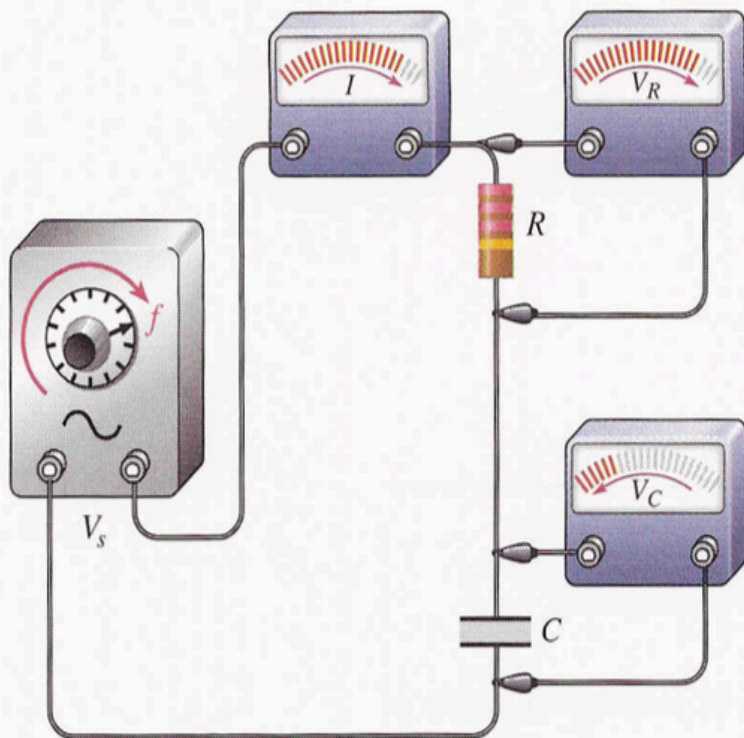
# Variation of Impedance & Phase Angle with Frequency




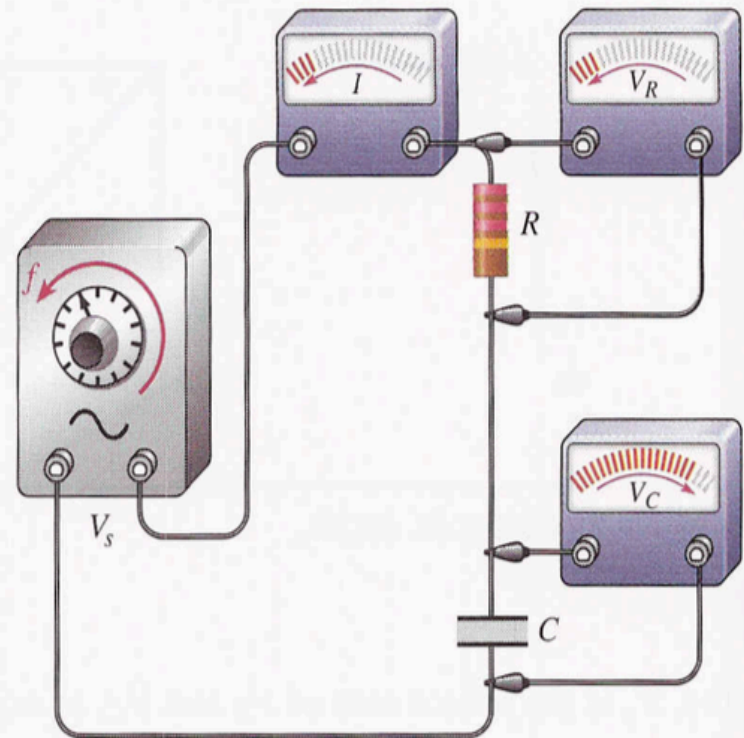(a) As frequency is increased,  $Z$  decreases as  $X_C$  decreases, causing  $I$  and  $V_R$  to increase and  $V_C$  to decrease.




(b) As frequency is decreased,  $Z$  increases as  $X_C$  increases, causing  $I$  and  $V_R$  to decrease and  $V_C$  to increase.
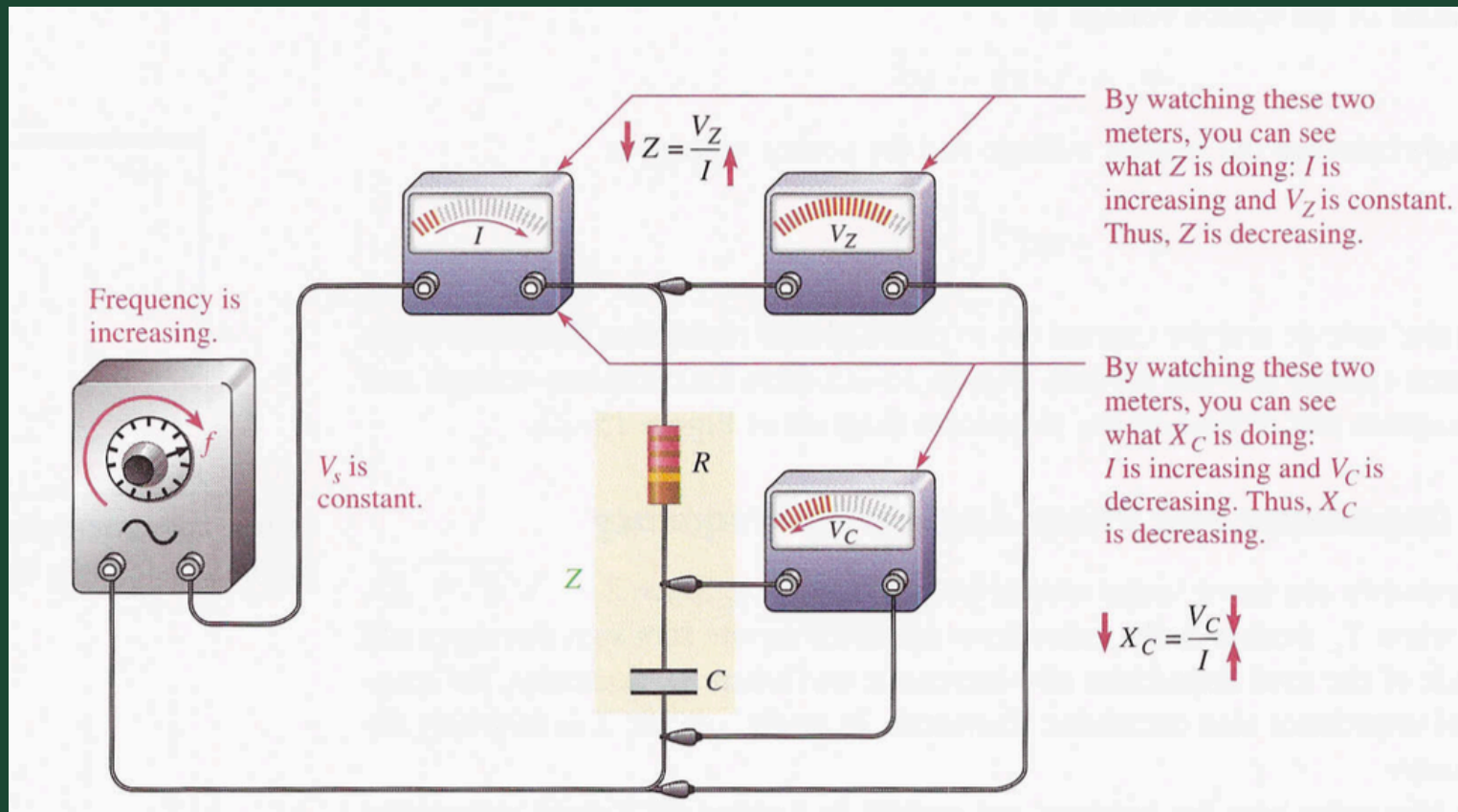
# Variation of Impedance & Phase Angle with Frequency (cont.)


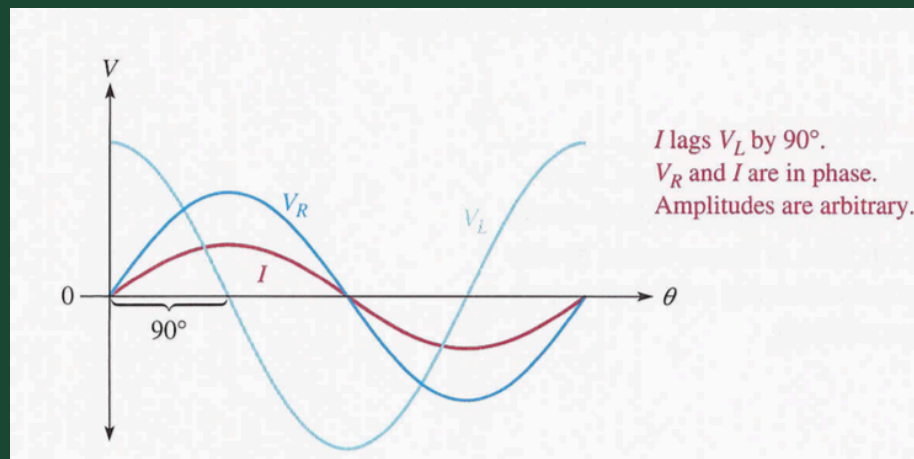
# Phase Relationships of RL Series Circuit

- ✓ In a series RL circuit, the current is the same through both the resistor and the inductor.
- ✓ Thus, the resistor voltage is in phase with the current and the inductor voltage leads the current by  $90^\circ$ .
- ✓ Therefore, there is a phase difference of  $90^\circ$  between the resistor voltage  $V_R$  and the inductor voltage  $V_L$  as shown below:



# Phase Relationships of RL Series Circuit (cont.)

- ✓ The sum of the voltage drops must equal to the applied voltage.
- ✓ However, since  $V_R$  and  $V_L$  are not in phase with each other, they must be added as phasor quantities with  $V_L$  leading  $V_R$  by  $90^\circ$ .
- ✓ Then  $V_s$  is the phasor sum of  $V_R$  and  $V_L$ :


$$V_s = V_R + jV_L$$

- ✓ In the polar form it can be expressed as:

$$V_s = \sqrt{V_R^2 + V_L^2} \angle \tan^{-1} \left( \frac{V_L}{V_R} \right)$$
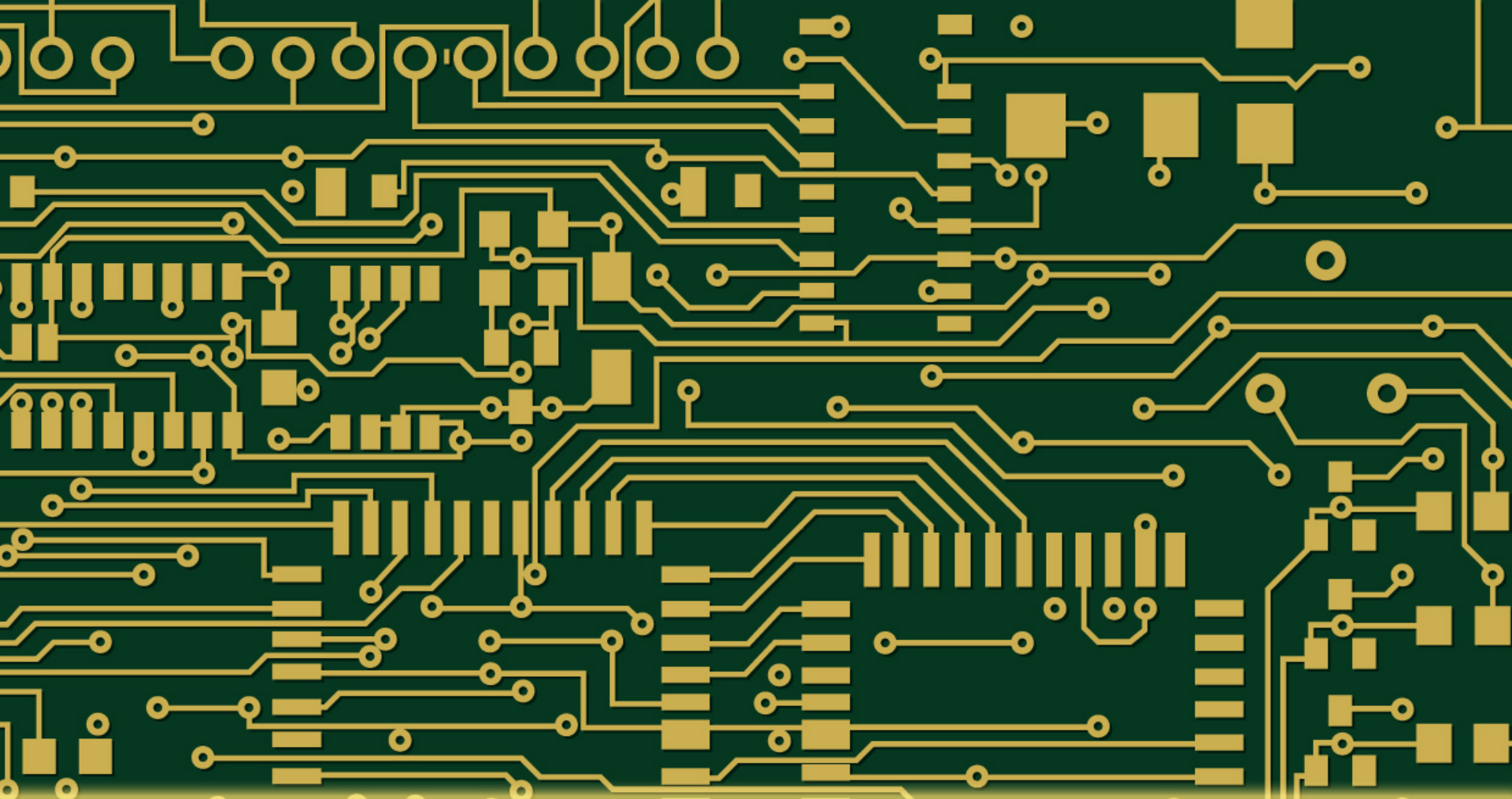
# Variation of Impedance & Phase Angle with Frequency


- ✓ As we know inductive reactance varies directly with frequency.
- ✓ When  $X_L$  increases, the magnitude of the total impedance also increases and when  $X_L$  decreases the magnitude of the total impedance decreases.
- ✓ Thus,  $Z$  is directly dependent in frequency.
- ✓ The phase angle  $\theta$  also varies directly with frequency because  $\theta = \tan^{-1} (X_L/R)$ . As  $X_L$  increases with frequency so does  $\theta$  and vice versa.




# RC with Lag & Lead Current
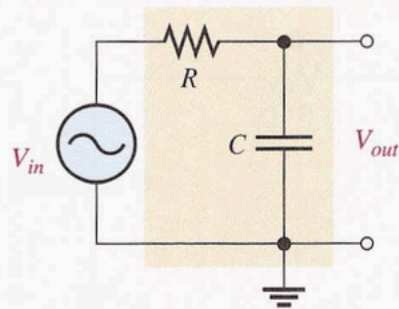
# RC Lag Circuit


- ✓ An RC lag circuit is a phase shift circuit in which the output voltage lags the input voltage by a specified amount.



(a) A basic RC lag circuit

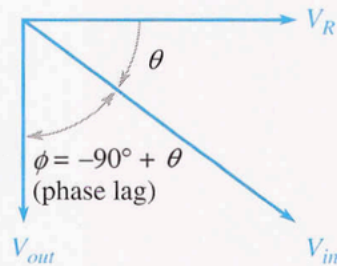

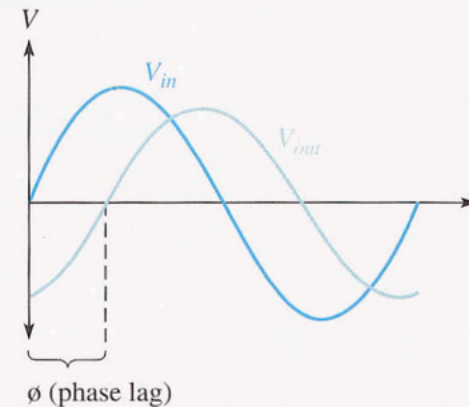(b) Phasor voltage diagram showing the phase lag between  $V_{in}$  and  $V_{out}$



(c) Input and output voltage waveforms



# RC Lag Circuit (cont.)

## ✓ Phase Difference Between Input and Output:

- ✓  $\theta$  is the phase angle between  $I$  and  $V_{in}$ .
- ✓ The angle between  $V_{out}$  and  $V_{in}$  is designated  $\phi$  and is developed as follows:
- ✓ The polar expressions for the input voltage and the current are  $V_{in} \angle 0^\circ$  and  $0 < \theta$  respectively.
- ✓ The output voltage in polar form is:

$$V_{out} = (I \angle \theta)(X_C \angle -90^\circ) = IX_C \angle (-90^\circ + \theta)$$

- ✓ The angle  $\phi$  between the input and output is:


$$\phi = -90 + \tan^{-1}\left(\frac{X_C}{R}\right)$$

- ✓ This angle can also be expressed as:

$$\phi = -\tan^{-1}\left(\frac{R}{X_C}\right)$$
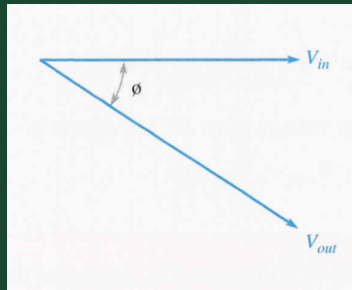
# RC Lag Circuit (cont.)

- ✓ This angle is always negative, indicating that the output voltage lags the input voltage as shown below:



- ✓ To evaluate the output voltage in terms of its magnitude, visualize the RC lag circuit as a voltage divider.


$$V_{out} = \left( \frac{X_C}{\sqrt{R^2 + X_C^2}} \right) V_{in}$$

- ✓ The phasor expression for the output voltage of an RC lag circuit is:

$$V_{out} = V_{out} \angle \phi$$

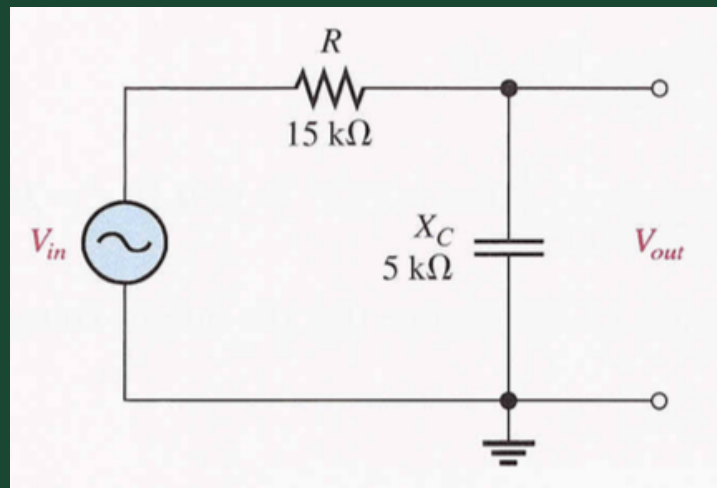
# Example #6

- ✓ Determine the amount of phase lag from input to output in following lag circuit:


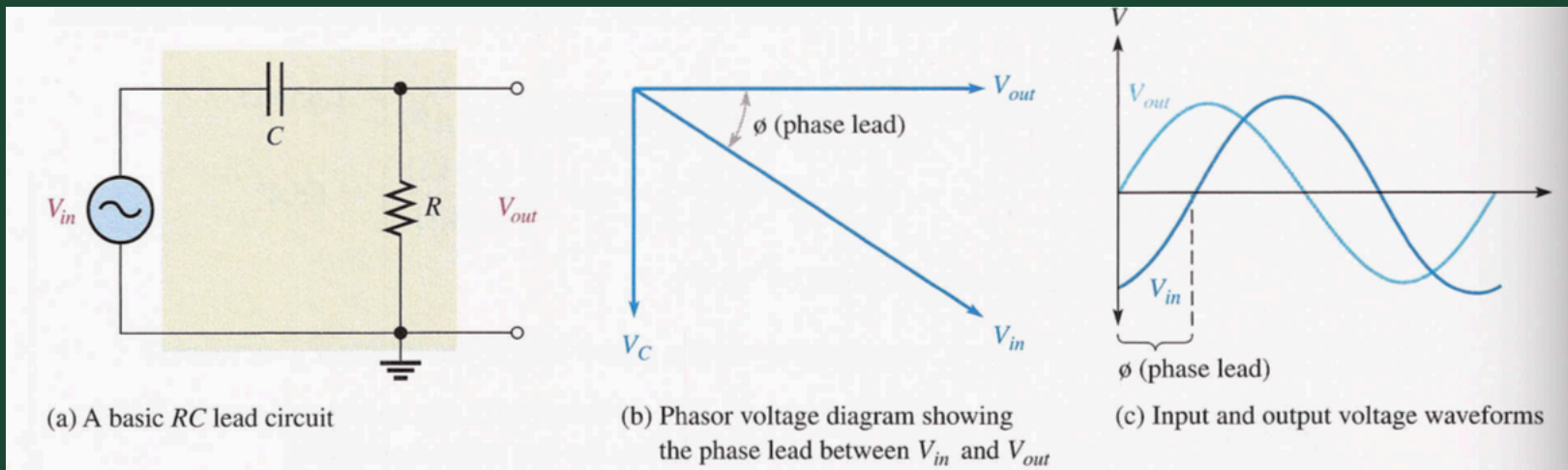
# RC Lead Circuit

- ✓ An RC lead circuit is a phase shift circuit in which the output voltage leads the input voltage by a specified amount.
- ✓ When the output of a series RC circuit is taken across the resistor rather than across the capacitor it becomes a lead circuit.




# Phase Difference b/w Input & Output

- ✓ In series RC circuit, the current leads the input voltage.
- ✓ Also the resistor voltage is in phase with the current.
- ✓ Since the output voltage is taken across the resistor, the output leads the input.
- ✓ The amount of phase difference b/w the input and output and the magnitude of the output voltage in the lead circuit are dependent on the relative values of the resistance and the capacitive reactance.
- ✓ When the input voltage is assigned a reference angle of  $0^\circ$ , the angle of the output voltage is the same as  $\theta$  because the resistor voltage and the current are in phase with each other.
- ✓ Therefore, since  $\phi = \theta$ , the expression is: 
$$\phi = \tan^{-1}\left(\frac{X_C}{R}\right)$$
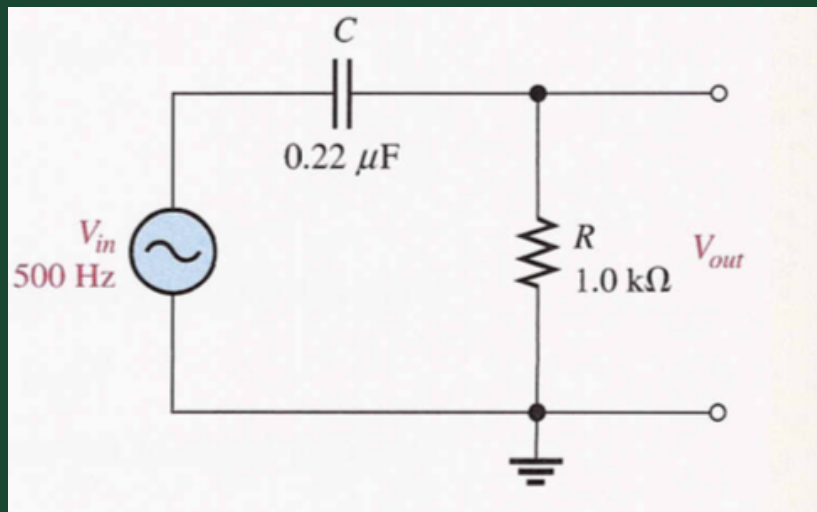
# Example #7

- ✓ Calculate the output phase angle for following circuit:




# Magnitude of the Output Voltage

- ✓ The voltage divider formula for the RC lead circuit is:

$$V_{out} = \left( \frac{R}{\sqrt{R^2 + X_C^2}} \right) V_{in}$$

- ✓ The expression for the output voltage in phasor form is:

$$V_{out} = V_{out} \angle \phi$$

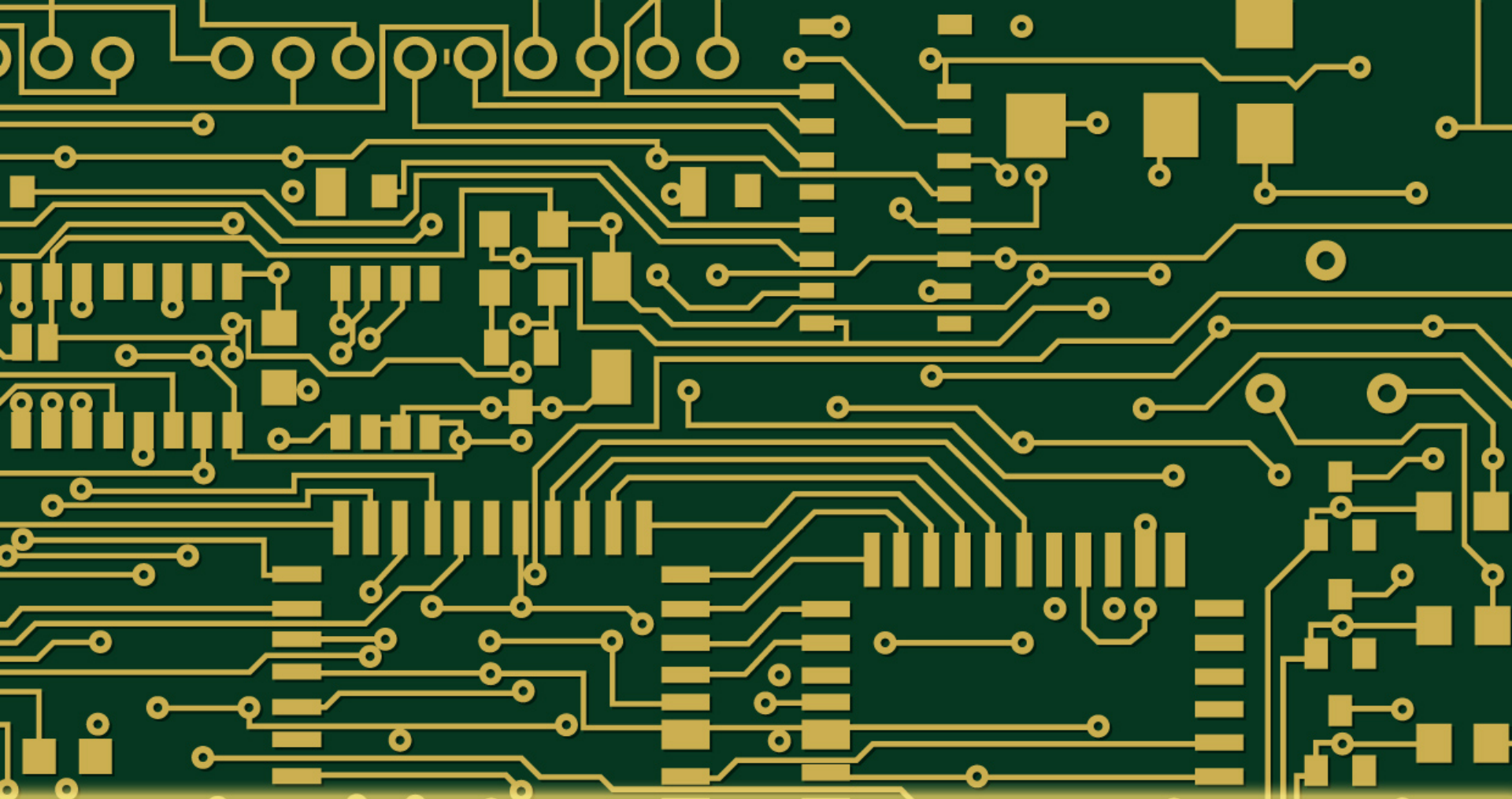


# RL with Lag & Lead Current



# RL Lead Circuit

- ✓ An RL lead circuit is a phase shift circuit in which the output voltage leads the input voltage by a specified amount.
- ✓ The source voltage is the input  $V_{in}$ .
- ✓ As  $\theta$  is the angle between the current and the input voltage, it is also the angle between the resistor voltage and the input voltage because  $V_R$  and  $I$  are in phase.
- ✓ Since  $V_L$  leads  $V_R$  by  $90^\circ$ , the phase angle between the inductor voltage and the input voltage is the difference between  $90^\circ$  and  $\theta$ .
- ✓ The inductor voltage is the output; it leads the input and thus creating a basic lead circuit.

# RL Lead Circuit (cont.)

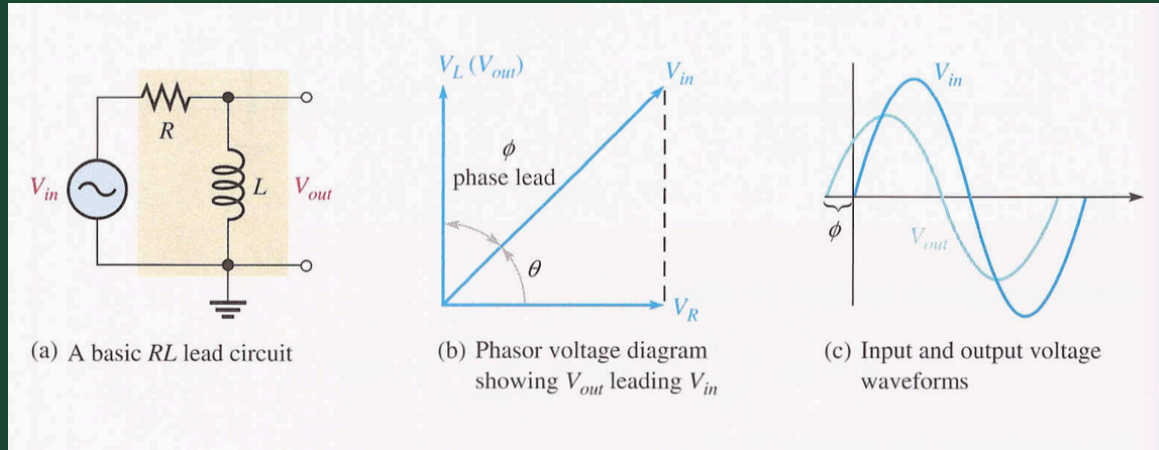

- ✓ Phase Difference B/w Input and Output:
- ✓ The polar expressions for the input voltage and the current are  $V_{in} \angle 0^\circ$  and  $I \angle -\theta$  respectively.
- ✓ The output voltage in polar form is:

$$V_{out} = (I \angle -\theta)(X_L \angle 90^\circ) = IX_L \angle (90^\circ - \theta)$$

# RL Lead Circuit (cont.)

- ✓ The angle  $\phi$  between the input and output is:

$$\phi = 90 - \tan^{-1}\left(\frac{X_L}{R}\right) \quad \text{or} \quad \phi = \tan^{-1}\left(\frac{R}{X_L}\right)$$

- ✓ Magnitude of the Output Voltage:
- ✓ The voltage divider formula is:


$$V_{out} = \left(\frac{X_L}{\sqrt{R^2 + X_L^2}}\right) V_{in}$$

- ✓ The phasor expression for the output voltage of an RL lead circuit is:

$$V_{out} = V_{out} \angle \phi$$

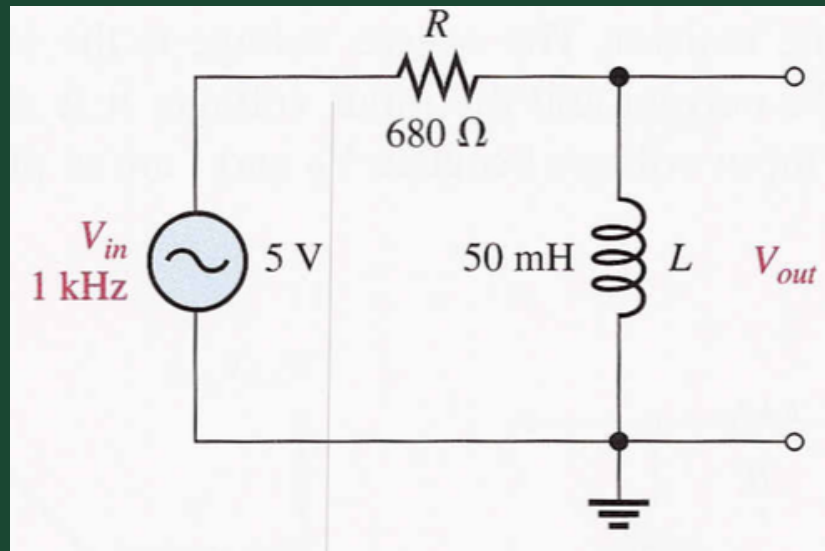
# Example #8

- ✓ For the lead circuit shown below, determine the output voltage in phasor form when the input voltage has an rms value of 5V. Draw the input and output voltage waveforms showing their peak values.
- ✓ The inductive  $X_L$  is  $314\Omega$ .



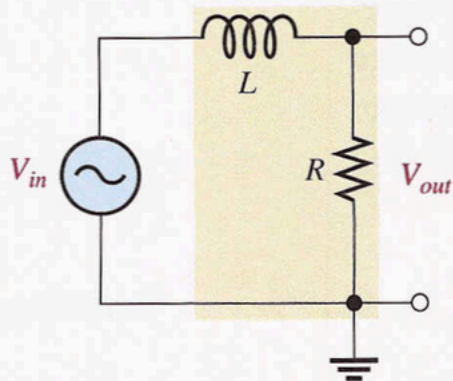
# RL Lag Circuit


- ✓ An RL lag circuit is a phase shift circuit in which the output voltage lags the input voltage by a specified amount.
- ✓ When the output of a series RL circuit is taken across the resistor rather than the inductor, it becomes a lag circuit.



(a) A basic *RL* lag circuit

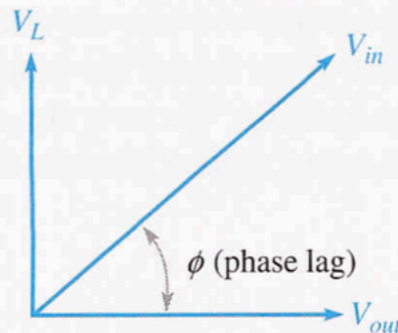

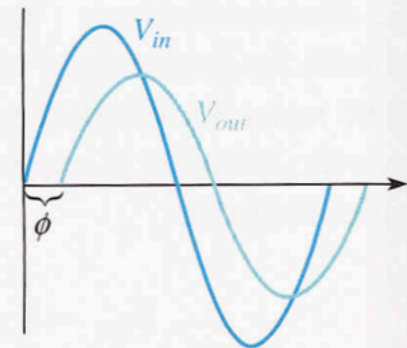(b) Phasor voltage diagram showing phase lag between  $V_{in}$  and  $V_{out}$



(c) Input and output waveforms

# RL Lag Circuit (cont.)

- ✓ Phase Difference b/w Input & Output:
- ✓ Since the output voltage is taken across the resistor, the output lags the input.
- ✓ When the input voltage is assigned a reference angle of  $0^\circ$ , the angle of the voltage with respect to the input voltage equals  $\theta$  because the resistor voltage and the current are in phase with each other.
- ✓ The expression for the angle is:

$$\phi = -\tan^{-1}\left(\frac{X_L}{R}\right)$$

# RL Lag Circuit (cont.)

- ✓ Magnitude of the Output Voltage:
- ✓ The voltage divider formula is:


$$V_{out} = \left( \frac{R}{\sqrt{R^2 + X_L^2}} \right) V_{in}$$

- ✓ The expression for the output voltage in phasor form is:


$$V_{out} = V_{out} \angle \phi$$
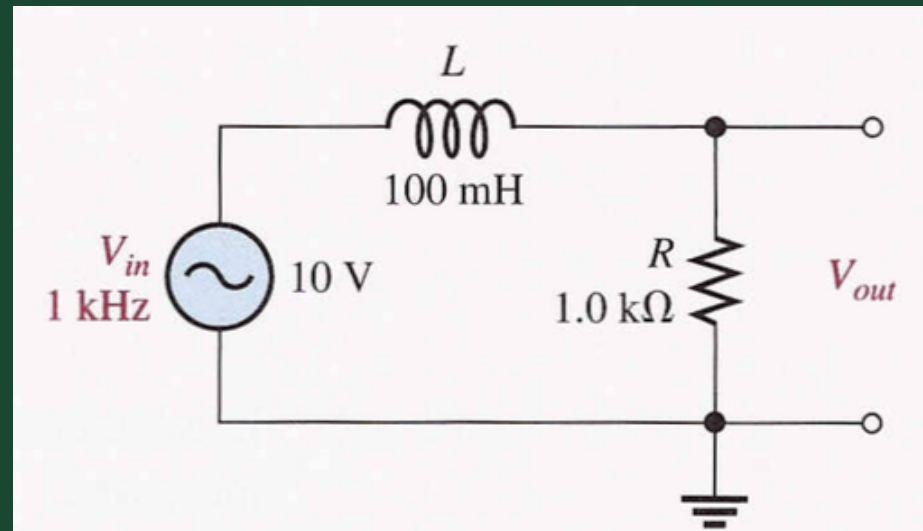
# Example #9

- ✓ The input voltage in the figure below, has an rms value of 10V. Determine the phasor expression for the output voltage. Draw the input and output voltage waveforms.
- ✓ The inductive  $X_L$  is  $628\Omega$ .





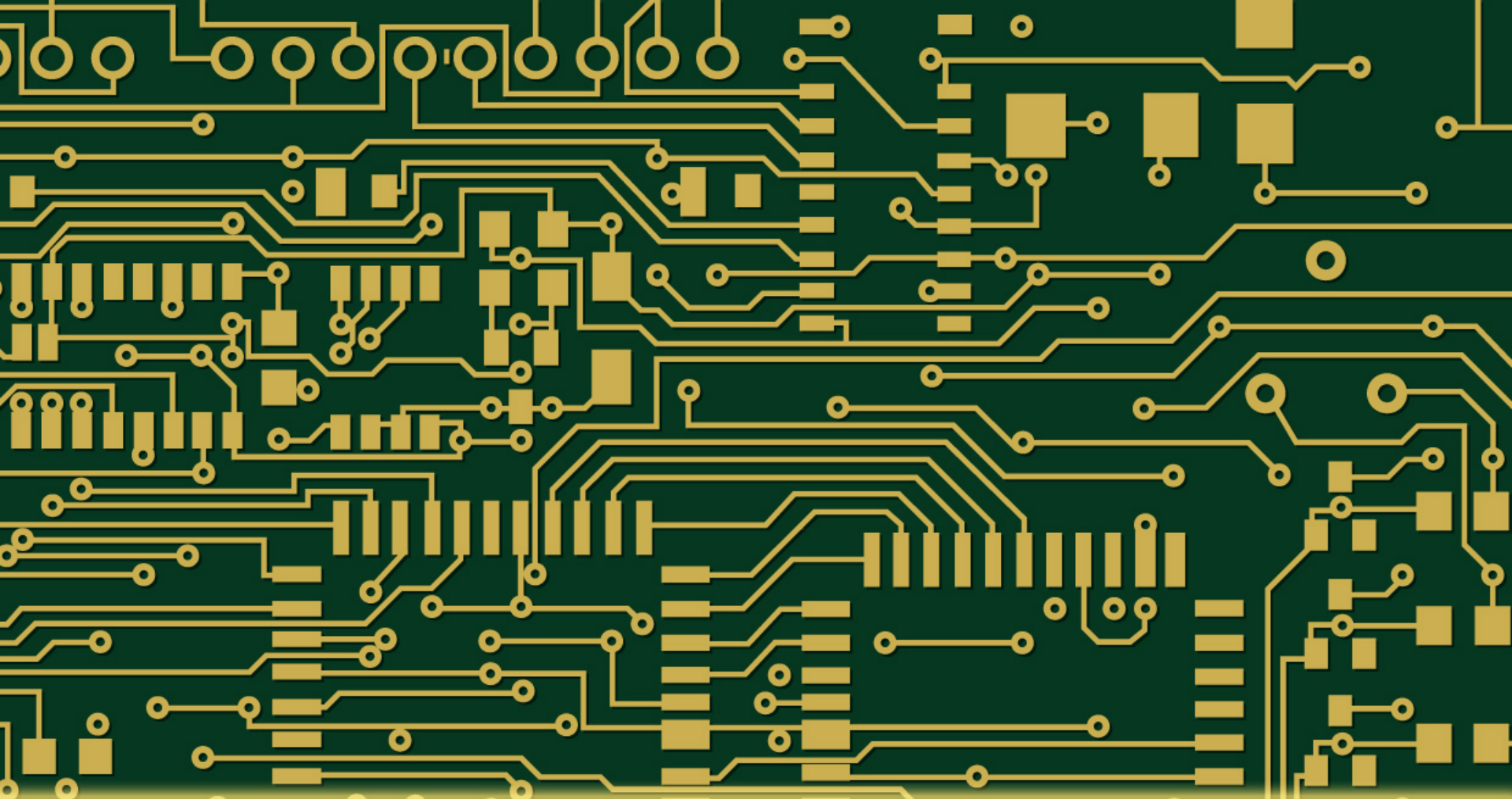

**Thank You**