

29/05/18 - MONDAY


= LECTURE #8 :-

EXAMPLE #1

Total admittance = ?

Convert it to total impedance = ?

Phasors diagram = ?

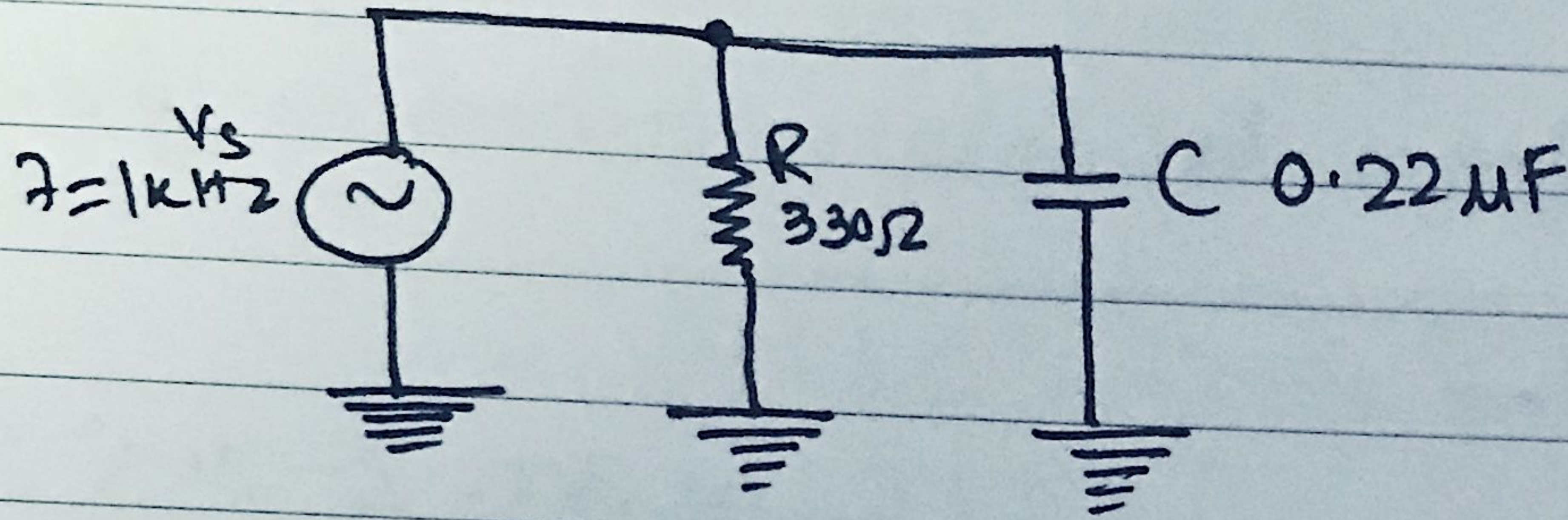

Soln-

The capacitive reactance = $X_C = \frac{1}{2\pi fC}$

$$= \frac{1}{2 \times \pi \times 1 \times 10^3 \times 0.22 \times 10^{-6}}$$

$$X_C \Rightarrow 723 \Omega$$

The capacitive susceptance magnitude = $B_C = \frac{1}{X_C}$

$$= \frac{1}{723} \Rightarrow 1.38 \text{ ms}$$

$$G = \frac{1}{R} \Rightarrow \frac{1}{330 \Omega} \Rightarrow 3.03 \text{ ms}$$


The total admittance is

$$Y_{\text{tot}} = G + jB_C \Rightarrow (3.03 + j1.38) \text{ ms}$$

In polar form $\Rightarrow Y_{\text{tot}} = \sqrt{G^2 + B_C^2} \angle \tan^{-1}\left(\frac{B_C}{G}\right)$

$$= \sqrt{(3.03)^2 + (1.38)^2} \angle \tan^{-1}\left(\frac{1.38}{3.03}\right)$$
$$Y_{\text{tot}} \Rightarrow 3.33 \angle 24.5^\circ \text{ ms}$$

The admittance phasor diagram is:-

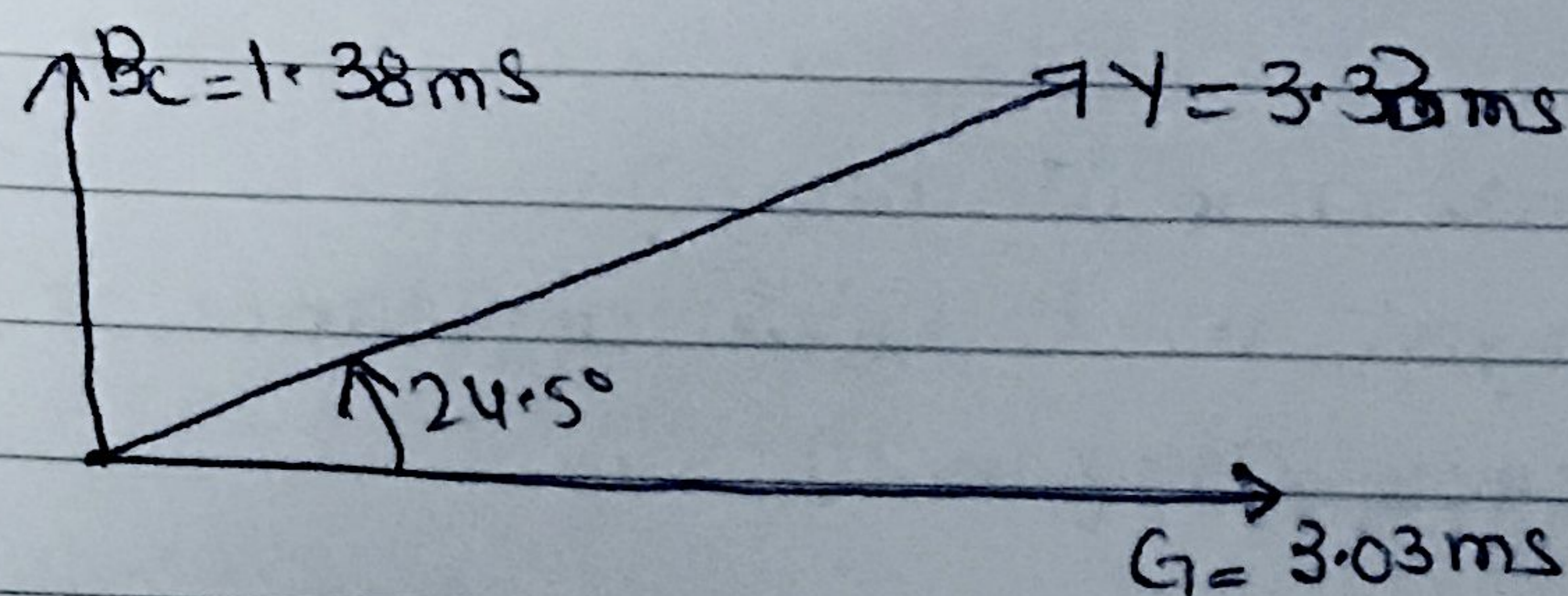


Convert total admittance to total impedance as follows:

$$Z_{tot} = \frac{1}{Y_{tot}}$$

$$= \frac{1}{3.33 \text{ mS} \angle 24.5^\circ} \Rightarrow 300 \angle -24.5^\circ \Omega$$

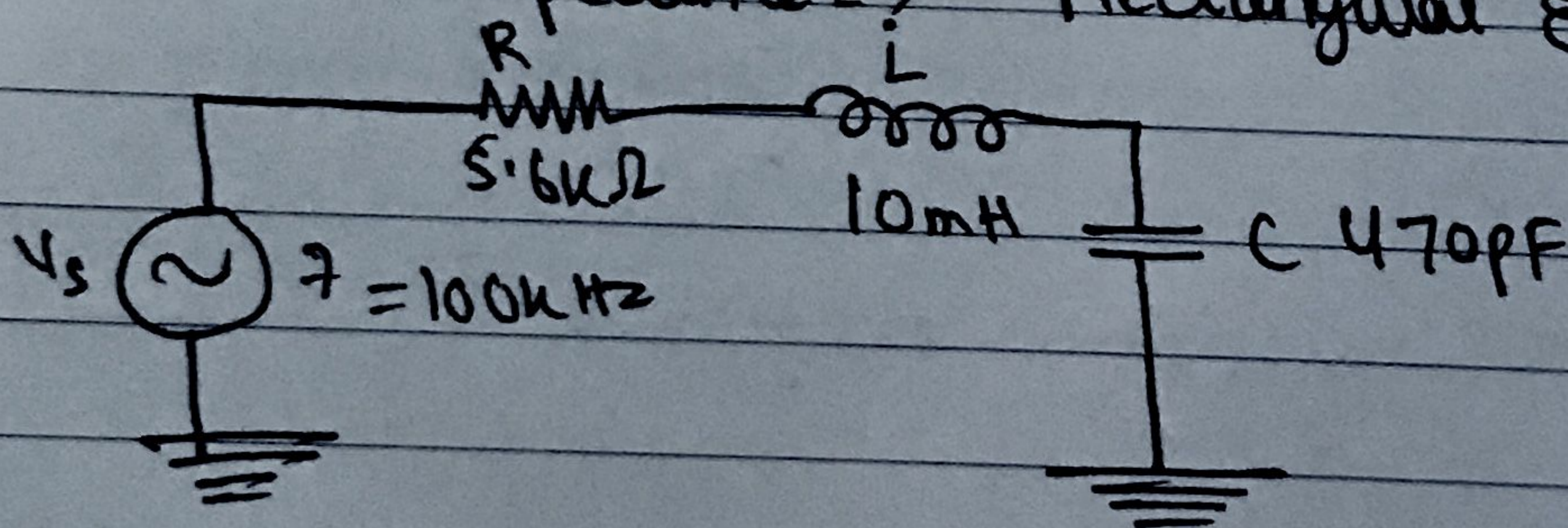EXAMPLE #2:

Total impedance = ? Rectangular & Polar = ?



Solve

X_C & $X_L = ?$

$$X_C = \frac{1}{2\pi fC} = \frac{1}{2 \times \pi \times 100 \times 10^3 \times 470 \times 10^{-12}}$$

$$X_C \Rightarrow 3.39 \text{ k}\Omega$$

$$X_L = 2\pi fL = 2\pi \times 100 \times 10^3 \times 10 \times 10^{-3}$$

$$X_L \Rightarrow 6.28 \text{ k}\Omega$$

In this case X_L is greater than X_C and thus the circuit is more inductive than capacitive.

The magnitude of total reactance is, $X_{tot} = |X_L - X_C|$
 $= |6.28 \text{ k}\Omega - 3.39 \text{ k}\Omega| \Rightarrow 2.89 \text{ k}\Omega$ inductive

The impedance in rectangular form is:

$$\begin{aligned}\bar{Z} &= R + (jX_L - jX_C) \\ &= 5.6k\Omega + (j6.28k\Omega - j3.39k\Omega) \\ \bar{Z} &\Rightarrow 5.6k\Omega + j2.89k\Omega\end{aligned}$$


The impedance in polar form is:

$$\begin{aligned}\bar{Z} &= \sqrt{R^2 + X_{tot}^2} \angle \tan^{-1}\left(\frac{X_{tot}}{R}\right) \\ &= \sqrt{(5.6k\Omega)^2 + (2.89k\Omega)^2} \angle \tan^{-1}\left(\frac{2.89k}{5.6k}\right) \\ \bar{Z} &= 6.30 \angle 27.3^\circ k\Omega\end{aligned}$$

The positive angle shows that circuit is inductive.

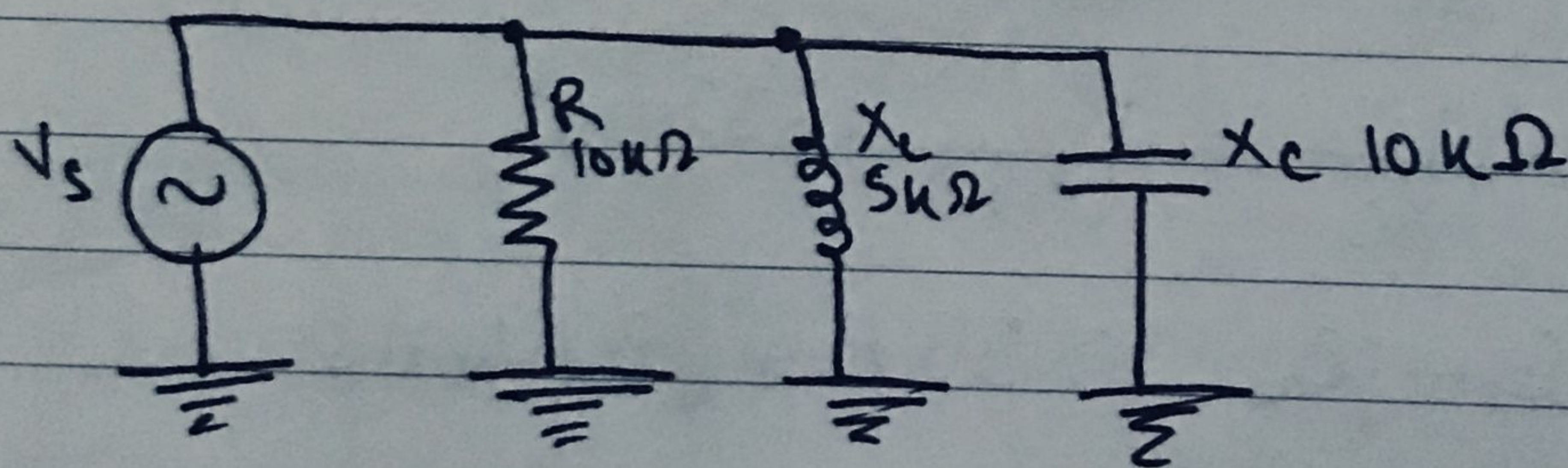EXAMPLE #3:

conductance, capacitive susceptance, inductive susceptance = ?
total admittance = ?



Solve

$$\bar{G} = \frac{1}{R \angle 0^\circ} = \frac{1}{10 \angle 0^\circ k\Omega} \Rightarrow 100 \angle 0^\circ \mu S$$

$$\bar{B}_C = \frac{1}{X_C \angle -90^\circ} = \frac{1}{10 \angle -90^\circ k\Omega} \Rightarrow 100 \angle 90^\circ \mu S$$

$$\bar{B}_L = \frac{1}{X_L \angle 90^\circ} = \frac{1}{5 \angle 90^\circ k\Omega} \Rightarrow 200 \angle -90^\circ \mu S$$


$$\begin{aligned}\bar{Y}_{tot} &= G + jB_C - jB_L = 100 \mu S + j100 \mu S - j(200 \mu S) \\ &= 100 \mu S - j100 \mu S \Rightarrow 141.4 \angle -45^\circ \mu S\end{aligned}$$

From Y_{tot} you can determine Z_{tot} .

$$Z_{tot} = \frac{1}{Y_{tot}} = \frac{1}{141.4 \angle -45^\circ \mu S} \\ \Rightarrow 7.07 \angle 45^\circ k\Omega$$

EXAMPLE #4

parallel \rightarrow Series Circuit

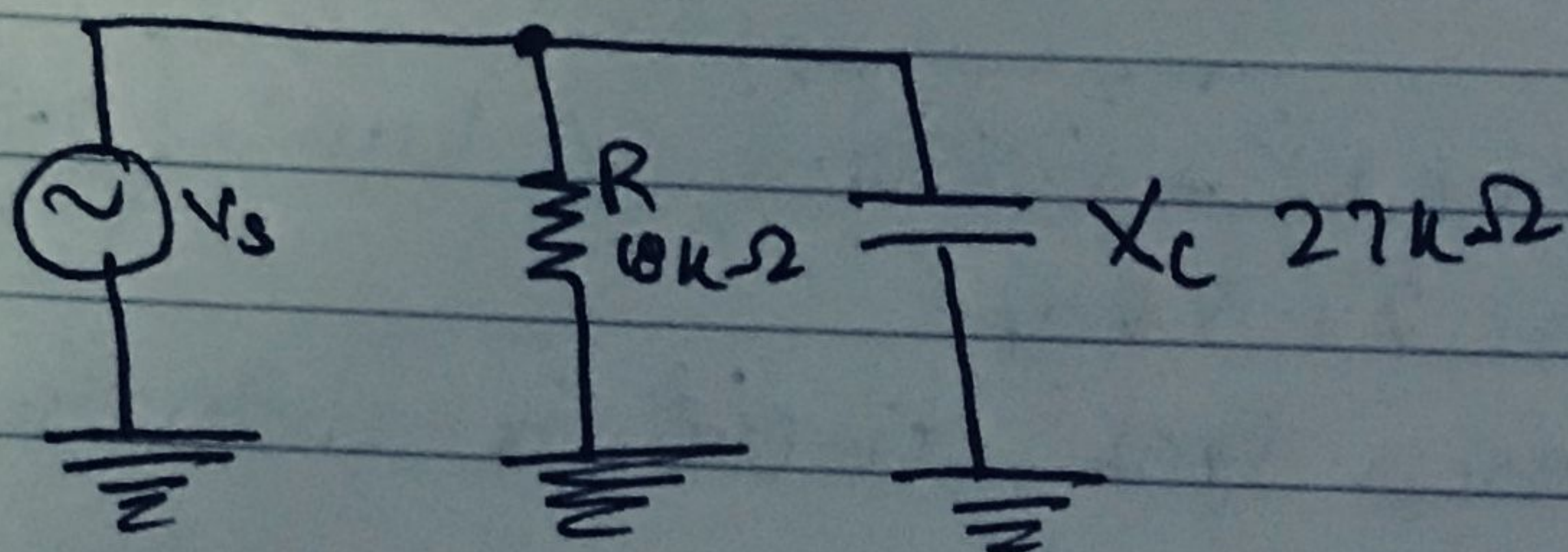

Soln

First, Find the admittance of the parallel circuit as follows:

$$G = \frac{1}{R} = \frac{1}{18 k\Omega} \Rightarrow 55.6 \mu S$$

$$B_C = \frac{1}{X_C} = \frac{1}{27 k\Omega} \Rightarrow 37.0 \mu S$$

$$\bar{Y} = G + jB_C \Rightarrow 55.6 + j37.0 \mu S$$

Converting to polar form yields

$$\bar{Y} = \sqrt{G^2 + B_C^2} \angle \tan^{-1} \left(\frac{B_C}{G} \right)$$

$$= \sqrt{(55.6 \mu)^2 + (37.0 \mu)^2} \angle \tan^{-1} \left(\frac{37.0 \mu}{55.6 \mu} \right)$$

$$\bar{Y} = 66.8 \angle 33.6^\circ \mu S$$

Then, total impedance is

$$\bar{Z}_{tot} = \frac{1}{\bar{Y}} = \frac{1}{66.8 \angle 33.6^\circ} \Rightarrow 15.0 \angle -33.6^\circ k\Omega$$

Converting to rectangular yields.


$$\bar{Z}_{tot} = Z \cos \theta - j Z \sin \theta$$

$$= R_{eq} - j X_{c(eq)}$$

$$= 15.0 \text{ k}\Omega \cos(-33.6^\circ) - j 15.0 \text{ k}\Omega \sin(-33.6^\circ)$$


$$\bar{Z}_{tot} \Rightarrow 12.5 \text{ k}\Omega - j 8.31 \text{ k}\Omega$$

The equivalent circuit is,

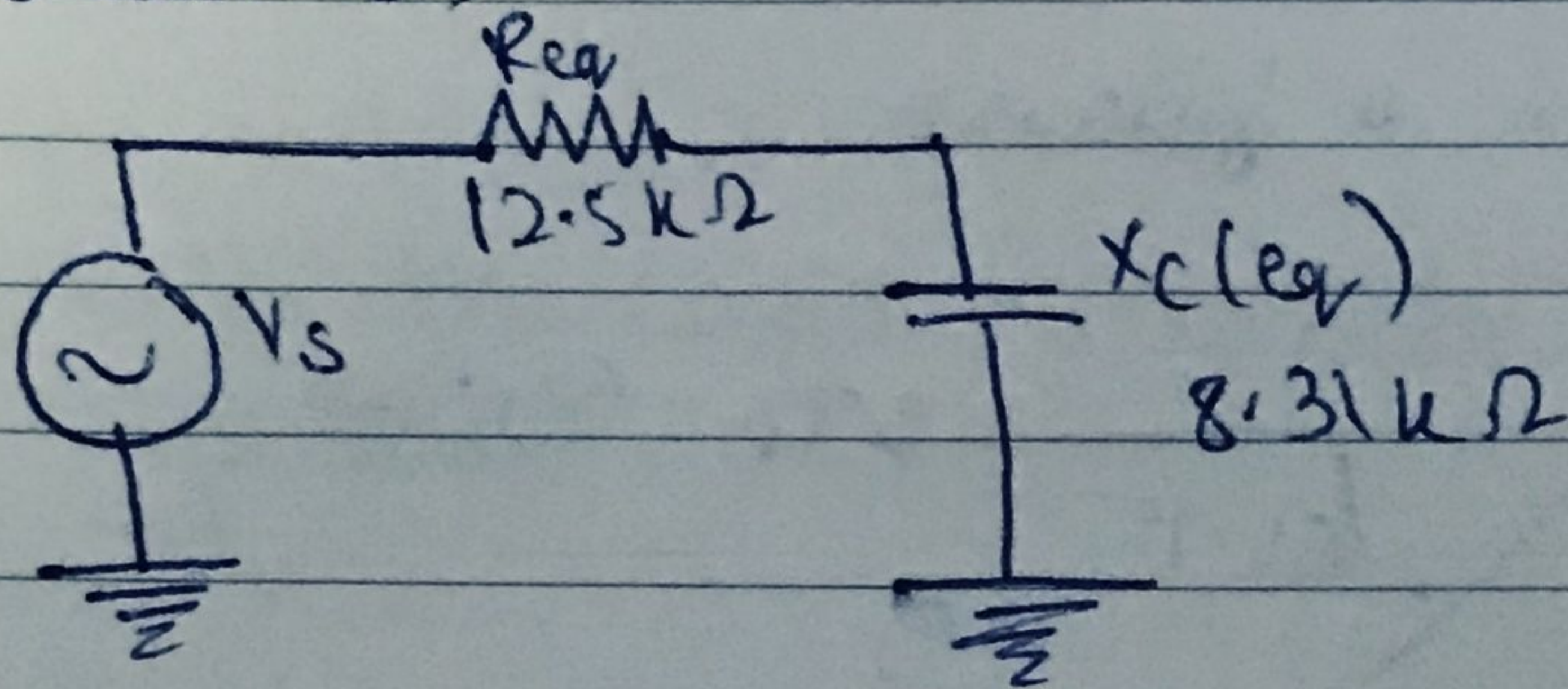

EXAMPLE #5:-

Each current & voltage = ?

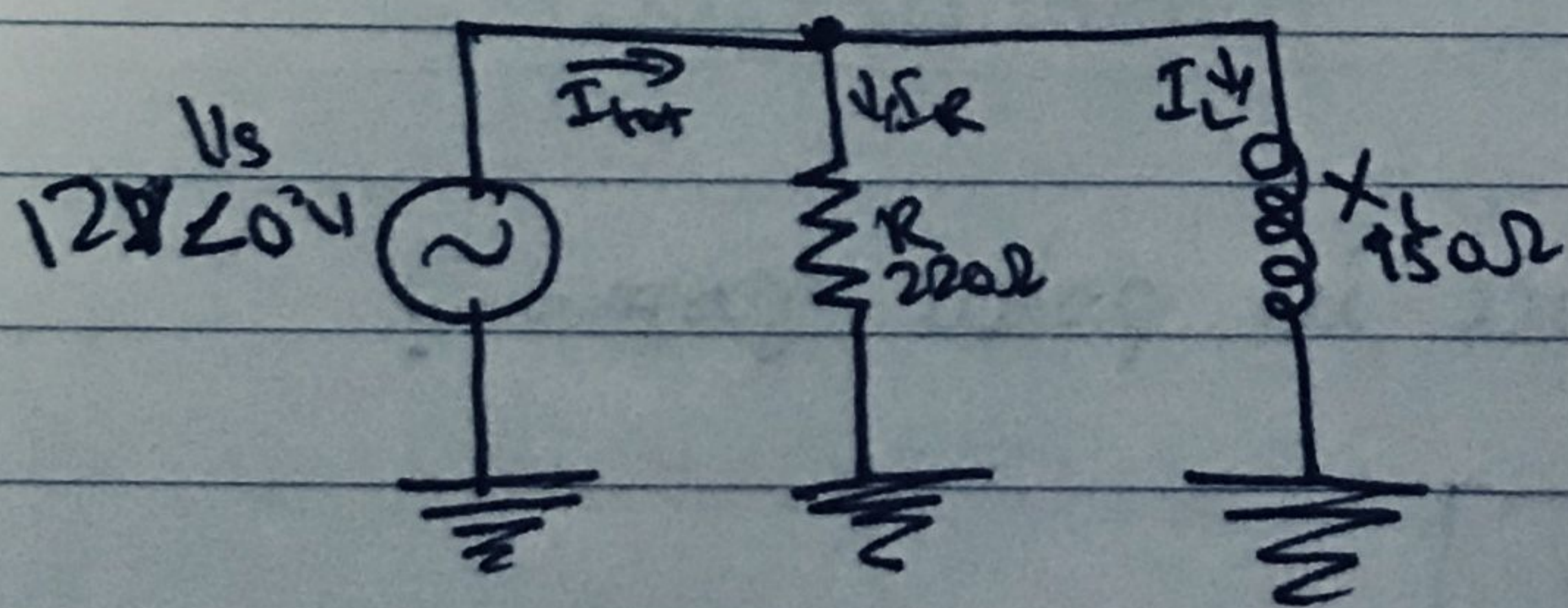

SOL:-

$$I_R = \frac{V_s}{R} = \frac{12 \angle 0^\circ \text{ V}}{220 \angle 0^\circ \Omega} \Rightarrow 54.5 \angle 0^\circ \text{ mA}$$

$$I_L = \frac{V_s}{X_L} = \frac{12 \angle 0^\circ \text{ V}}{150 \angle 90^\circ \Omega} \Rightarrow 80 \angle -90^\circ \text{ mA}$$

$$I_{tot} = I_R - j I_L \\ = 54.5 \text{ mA} - j 80 \text{ mA}$$


I_{tot} to polar form yields

$$I_{tot} = \sqrt{I_R^2 + I_L^2} \angle -\tan^{-1}\left(\frac{I_L}{I_R}\right)$$

$$= \sqrt{(54.5\text{mA})^2 + (80\text{mA})^2} \angle -\tan^{-1}\left(\frac{80\text{mA}}{54.5\text{mA}}\right)$$


$$I_{tot} \Rightarrow 96.8 \angle -55.7^\circ \text{mA}$$

The phasor diagram is follows:-

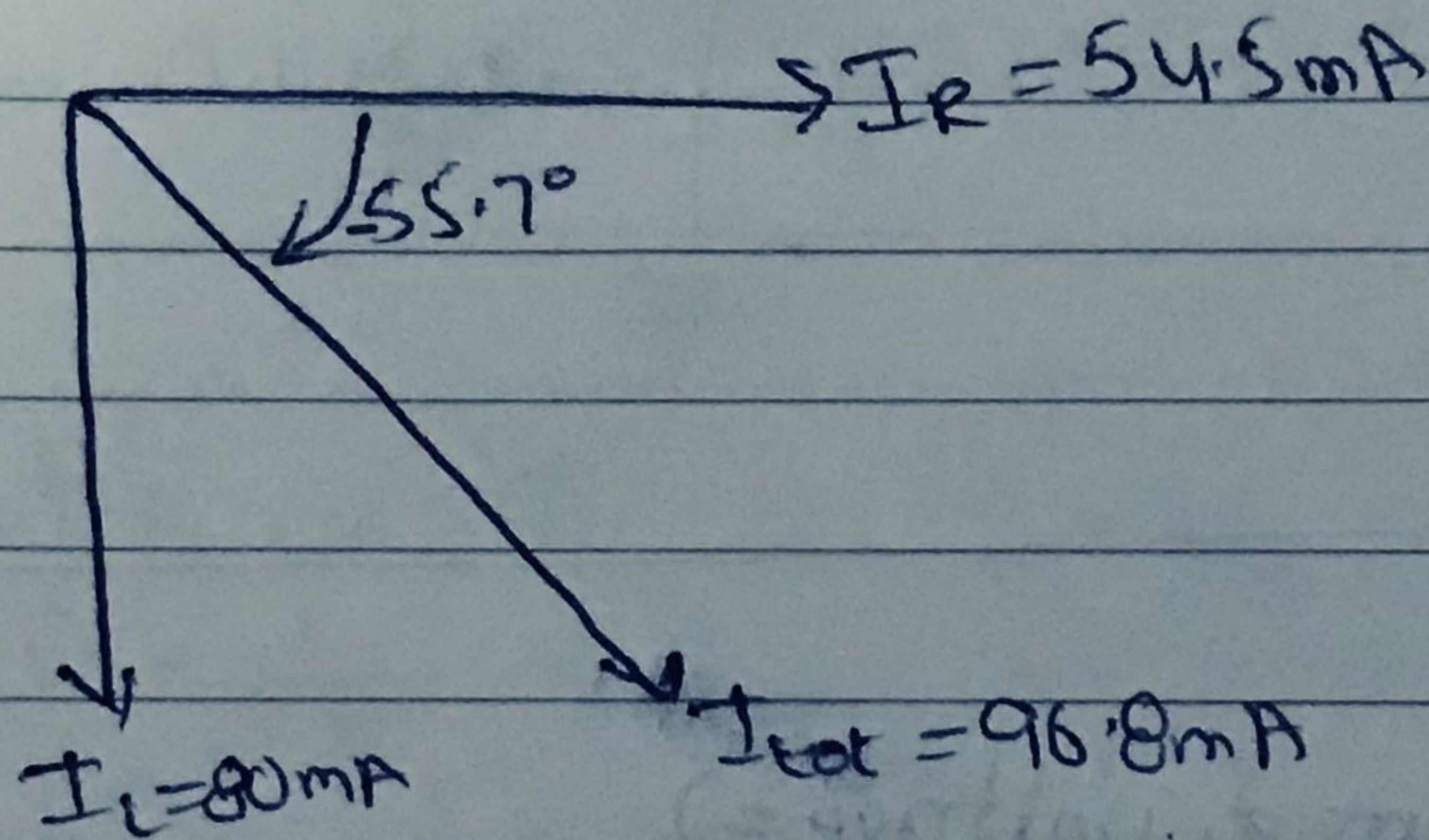

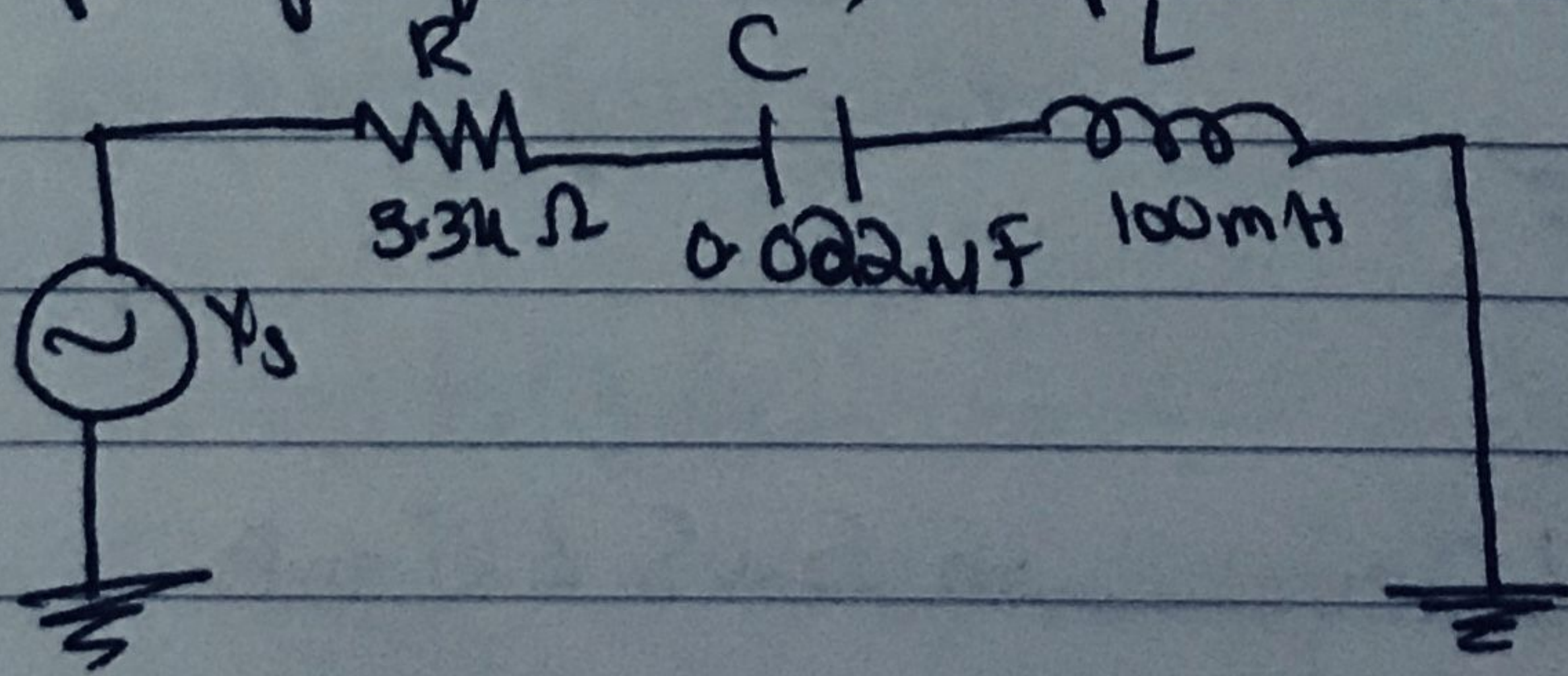EXAMPLE # 6:-

input frequencies, impedance in polar form = ?



a) $f = 1\text{kHz}$

Solve

$$X_C = \frac{1}{2\pi f C} = \frac{1}{2\pi \times 1 \times 10^3 \times 0.0022\mu}$$

$$X_C \Rightarrow 7.23\text{k}\Omega$$

$$X_L = 2\pi fL \Rightarrow 2\pi (1\text{kHz}) (100\text{mH})$$

$$X_L \Rightarrow 628\Omega$$

The circuit is clearly capacitive, and the impedance is

$$\bar{Z} = \sqrt{R^2 + (X_L - X_C)^2} \angle -\tan^{-1}\left(\frac{X_{\text{tot}}}{R}\right)$$

$$= \sqrt{(3.3\text{k}\Omega)^2 + (628\Omega - 7.23\text{k}\Omega)^2} \angle -\tan^{-1}\left(\frac{6.60\text{k}\Omega}{3.3\text{k}\Omega}\right)$$

$$\bar{Z} \Rightarrow 7.38 \angle -63.4^\circ \text{ k}\Omega$$

The negative sign for the angle is used to indicate that the circuit is capacitive.

b) $f = 3.5\text{kHz}$

Solve

$$X_C = \frac{1}{2\pi fC} = \frac{1}{2\pi (3.5\text{kHz}) (0.022\mu\text{F})}$$

$$X_C \Rightarrow 2.07\text{k}\Omega$$

$$X_L = 2\pi fL = 2\pi \times 3.5\text{kHz} \times 100\text{mH} \Rightarrow 2.20\text{k}\Omega$$


The circuit is very close to being purely resistive because X_C and X_L are nearly equal, but it is slightly inductive.

The impedance is,

$$\bar{Z} = \sqrt{(3.3\text{k}\Omega)^2 + (2.20\text{k}\Omega - 2.07\text{k}\Omega)^2} \angle \tan^{-1}\left(\frac{0.13\text{k}\Omega}{3.3\text{k}\Omega}\right)$$

$$\bar{Z} = 3.3 \angle 2.26^\circ \text{ k}\Omega$$

EXAMPLE #78

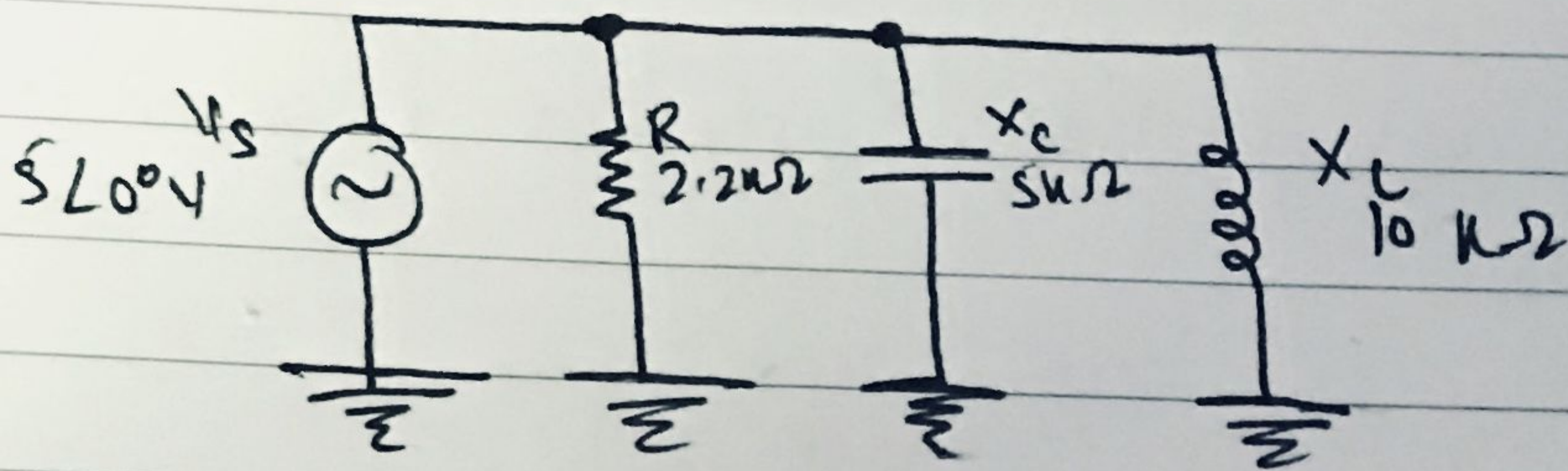

Soln

$$I_R = \frac{V_s}{R} = \frac{5\angle 0^\circ \text{ V}}{2.2\angle 0^\circ \text{ k}\Omega} \Rightarrow 2.27\angle 0^\circ \text{ mA}$$

$$I_c = \frac{V_s}{X_c} = \frac{5\angle 0^\circ \text{ V}}{5\angle -90^\circ \text{ k}\Omega} \Rightarrow 1\angle 90^\circ \text{ mA}$$

$$I_L = \frac{V_s}{X_L} = \frac{5\angle 0^\circ \text{ V}}{10\angle 90^\circ \text{ k}\Omega} \Rightarrow 0.5\angle -90^\circ \text{ mA}$$

The total current is the phasor sum of the branch currents.

$$\begin{aligned} I_{\text{tot}} &= I_R + I_c + I_L \\ &= 2.27\angle 0^\circ \text{ mA} + 1\angle 90^\circ \text{ mA} + 0.5\angle -90^\circ \text{ mA} \end{aligned}$$

$$\begin{aligned} I_{\text{tot}} &= 2.27 \text{ mA} + j1 \text{ mA} - j0.5 \text{ mA} \\ &\Rightarrow 2.27 + j0.5 \text{ mA} \end{aligned}$$

Converting to polar form yields,

$$\begin{aligned} I_{\text{tot}} &= \sqrt{I_R^2 + (I_c - I_L)^2} \angle \tan^{-1} \left(\frac{I_c - I_L}{I_R} \right) \\ &= \sqrt{(2.27 \text{ mA})^2 + (0.5 \text{ mA})^2} \angle \tan^{-1} \left(\frac{0.5 \text{ mA}}{2.27 \text{ mA}} \right) \end{aligned}$$

$$I_{\text{tot}} = 2.32\angle 12.4^\circ \text{ mA}$$

The total current is 2.32 mA leading V_s by 12.4°
The current phasor diagram is:

