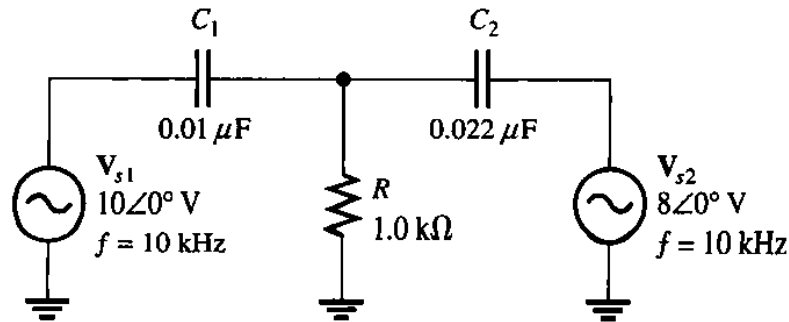


Example #1

Find the current in R of Figure 19–1 using the superposition theorem. Assume the internal source impedances are zero.



Step 1. Replace V_{s2} with its internal impedance (zero in this case), and find the current in R due to V_{s1} , as indicated in Figure 19–2.

$$X_{C1} = \frac{1}{2\pi f C_1} = \frac{1}{2\pi(10 \text{ kHz})(0.01 \mu\text{F})} = 1.59 \text{ k}\Omega$$

$$X_{C2} = \frac{1}{2\pi f C_2} = \frac{1}{2\pi(10 \text{ kHz})(0.022 \mu\text{F})} = 723 \Omega$$

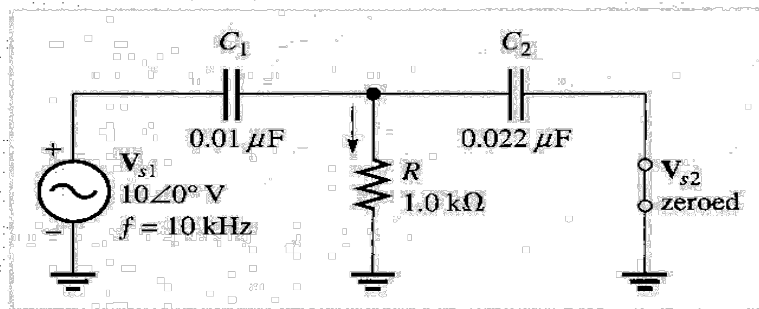


FIGURE 19–2

Looking from V_{s1} , the impedance is

$$\begin{aligned} Z &= X_{C1} + \frac{RX_{C2}}{R + X_{C2}} = 1.59 \angle -90^\circ \text{ k}\Omega + \frac{(1.0 \angle 0^\circ \text{ k}\Omega)(723 \angle -90^\circ \Omega)}{1.0 \text{ k}\Omega - j723 \Omega} \\ &= 1.59 \angle -90^\circ \text{ k}\Omega + 588 \angle -54.1^\circ \Omega \\ &= -j1.59 \text{ k}\Omega + 345 \Omega - j476 \Omega = 345 \Omega - j2.07 \text{ k}\Omega \end{aligned}$$

Converting to polar form yields

$$Z = 2.10 \angle -80.5^\circ \text{ k}\Omega$$


The total current from V_{s1} is

$$\mathbf{I}_{s1} = \frac{\mathbf{V}_{s1}}{\mathbf{Z}} = \frac{10 \angle 0^\circ \text{ V}}{2.10 \angle -80.5^\circ \text{ k}\Omega} = 4.76 \angle 80.5^\circ \text{ mA}$$

Use the current-divider formula. The current through R due to V_{s1} is

$$\begin{aligned} \mathbf{I}_{R1} &= \left(\frac{X_{C2} \angle -90^\circ}{R - jX_{C2}} \right) \mathbf{I}_{s1} = \left(\frac{723 \angle -90^\circ \Omega}{1.0 \text{ k}\Omega - j723 \Omega} \right) 4.76 \angle 80.5^\circ \text{ mA} \\ &= (0.588 \angle -54.9^\circ \Omega)(4.76 \angle 80.5^\circ \text{ mA}) = 2.80 \angle 25.6^\circ \text{ mA} \end{aligned}$$

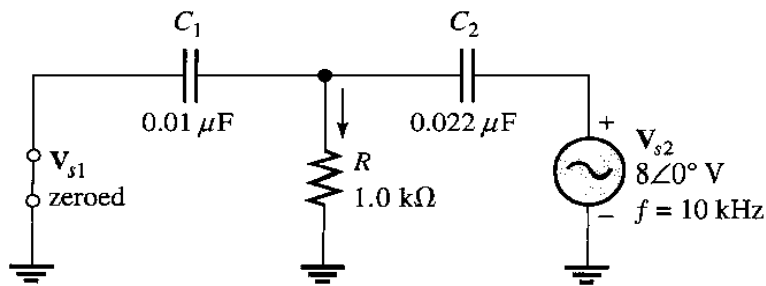Step 2. Find the current in R due to source V_{s2} by replacing V_{s1} with its internal impedance (zero), as shown in Figure 19-3.



▲ FIGURE 19-3

Looking from V_{s2} , the impedance is

$$\begin{aligned} \mathbf{Z} &= \mathbf{X}_{C2} + \frac{\mathbf{R}\mathbf{X}_{C1}}{\mathbf{R} + \mathbf{X}_{C1}} = 723 \angle -90^\circ \Omega + \frac{(1.0 \angle 0^\circ \text{ k}\Omega)(1.59 \angle -90^\circ \text{ k}\Omega)}{1.0 \text{ k}\Omega - j1.59 \text{ k}\Omega} \\ &= 723 \angle -90^\circ \Omega + 847 \angle -32.2^\circ \Omega \\ &= -j723 \Omega + 717 \Omega - j451 \Omega = 717 \Omega - j1174 \Omega \end{aligned}$$

Converting to polar form yields

$$\mathbf{Z} = 1376 \angle -58.6^\circ \Omega$$

The total current from V_{s2} is

$$\mathbf{I}_{s2} = \frac{\mathbf{V}_{s2}}{\mathbf{Z}} = \frac{8 \angle 0^\circ \text{ V}}{1376 \angle -58.6^\circ \Omega} = 5.81 \angle 58.6^\circ \text{ mA}$$

Use the current-divider formula. The current through R due to V_{s2} is

$$\begin{aligned} \mathbf{I}_{R2} &= \left(\frac{\mathbf{X}_{C1} \angle -90^\circ}{\mathbf{R} - j\mathbf{X}_{C1}} \right) \mathbf{I}_{s2} \\ &= \left(\frac{1.59 \angle -90^\circ \text{ k}\Omega}{1.0 \text{ k}\Omega - j1.59 \text{ k}\Omega} \right) 5.81 \angle 58.6^\circ \text{ mA} = 4.91 \angle 26.4^\circ \text{ mA} \end{aligned}$$

Step 3. Convert the two individual resistor currents to rectangular form and add to get the total current through R .

$$\mathbf{I}_{R1} = 2.80 \angle 25.6^\circ \text{ mA} = 2.53 \text{ mA} + j1.21 \text{ mA}$$

$$\mathbf{I}_{R2} = 4.91 \angle 26.4^\circ \text{ mA} = 4.40 \text{ mA} + j2.18 \text{ mA}$$

$$\mathbf{I}_R = \mathbf{I}_{R1} + \mathbf{I}_{R2} = 6.93 \text{ mA} + j3.39 \text{ mA} = 7.71 \angle 26.1^\circ \text{ mA}$$

Example #2:

Refer to Figure 19–15. Determine V_{th} for the circuit within the beige box as viewed from terminals A and B .

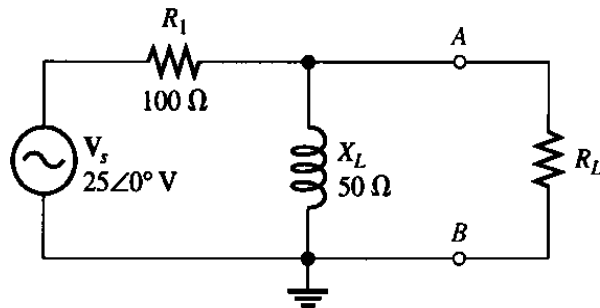


FIGURE 19–15


Solution Remove R_L and determine the voltage from A to B (V_{th}). In this case, the voltage from A to B is the same as the voltage across X_L . This is determined using the voltage-divider method.

$$\begin{aligned} V_L &= \left(\frac{X_L \angle 90^\circ}{R_1 + jX_L} \right) V_s \\ &= \left(\frac{50 \angle 90^\circ \Omega}{100 \Omega + j50 \Omega} \right) \\ &= \left(\frac{50 \angle 90^\circ \Omega}{112 \angle 26.6^\circ \Omega} \right) 25 \angle 0^\circ \text{ V} = 11.2 \angle 63.4^\circ \text{ V} \\ V_{th} &= V_{AB} = V_L = 11.2 \angle 63.4^\circ \text{ V} \end{aligned}$$

Example #3:

Find Z_{th} for the part of the circuit in Figure 19–18 that is within the beige box as viewed from terminals A and B . This is the same circuit used in Example 19–4.


FIGURE 19–18

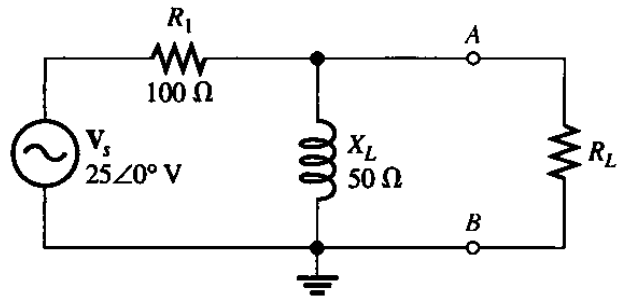

Solution First, replace V_s with its internal impedance (zero in this case), as shown in Figure 19–19. Looking in between terminals A and B , R_1 and X_L are in parallel. Thus,

$$\begin{aligned} Z_{th} &= \frac{(R_1 \angle 0^\circ)(X_L \angle 90^\circ)}{R_1 + jX_L} = \frac{(100 \angle 0^\circ \Omega)(50 \angle 90^\circ \Omega)}{100 \Omega + j50 \Omega} \\ &= \frac{(100 \angle 0^\circ \Omega)(50 \angle 90^\circ \Omega)}{112 \angle 26.6^\circ \Omega} = 44.6 \angle 63.4^\circ \Omega \end{aligned}$$

FIGURE 19–19

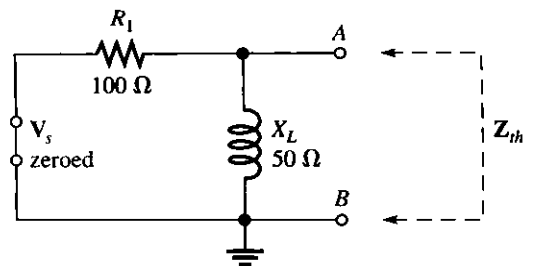

Example #4:

Refer to Figure 19–24. Draw the Thevenin equivalent for the circuit within the beige box as viewed from terminals *A* and *B*. This is the circuit used in Examples 19–4 and 19–7.

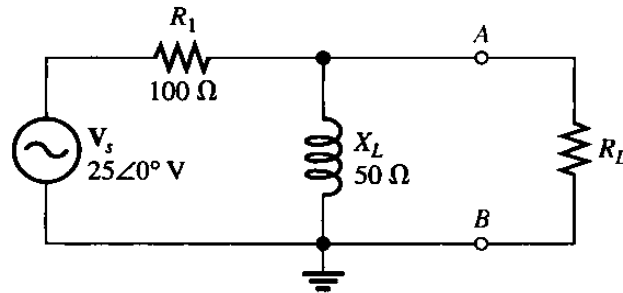


FIGURE 19–24

Solution From Examples 19–4 and 19–7, respectively, $V_{th} = 11.2 \angle 63.4^\circ \text{ V}$ and $Z_{th} = 44.6 \angle 63.4^\circ \Omega$. In rectangular form, the impedance is

$$Z_{th} = 20 \Omega + j40 \Omega$$

This form indicates that the impedance is a 20Ω resistor in series with a 40Ω inductive reactance. The Thevenin equivalent circuit is shown in Figure 19–25.


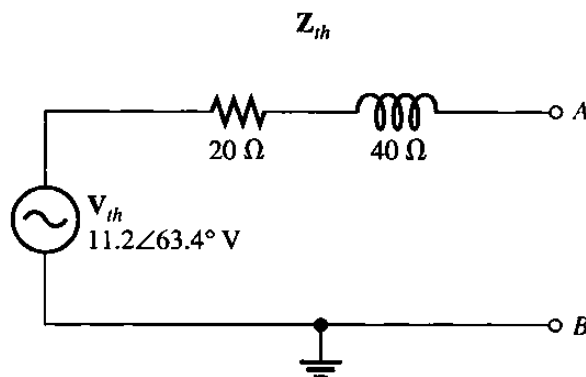


FIGURE 19–25

Example #5:


In Figure 19–33, determine I_n for the circuit as “seen” by the load resistor. The beige area identifies the portion of the circuit to be nortonized.

FIGURE 19–33

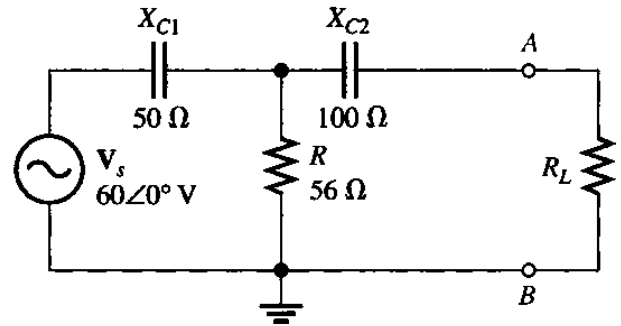

Solution Short the terminals A and B , as shown in Figure 19–34.

FIGURE 19–34

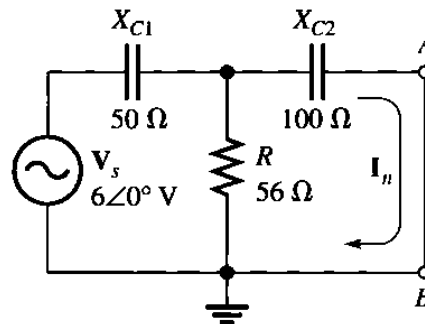

I_n is the current through the short and is calculated as follows. First, the total impedance viewed from the source is

$$\begin{aligned} \mathbf{Z} &= \mathbf{X}_{C1} + \frac{\mathbf{R}\mathbf{X}_{C2}}{\mathbf{R} + \mathbf{X}_{C2}} = 50\angle-90^\circ \Omega + \frac{(56\angle 0^\circ \Omega)(100\angle-90^\circ \Omega)}{56 \Omega - j100 \Omega} \\ &= 50\angle-90^\circ \Omega + 48.9\angle-29.3^\circ \Omega \\ &= -j50 \Omega + 42.6 \Omega - j23.9 \Omega = 42.6 \Omega - j73.9 \Omega \end{aligned}$$

Converting to polar form yields

$$\mathbf{Z} = 85.3\angle-60.0^\circ \Omega$$

Next, the total current from the source is

$$I_s = \frac{V_s}{Z} = \frac{6 \angle 0^\circ \text{ V}}{85.3 \angle -60.0^\circ \Omega} = 70.3 \angle 60.0^\circ \text{ mA}$$

Finally, apply the current-divider formula to get I_n (the current through the short between terminals A and B).

$$I_n = \left(\frac{R}{R + X_{C2}} \right) I_s = \left(\frac{56 \angle 0^\circ \Omega}{56 \Omega - j100 \Omega} \right) 70.3 \angle 60.0^\circ \text{ mA} = 34.4 \angle 121^\circ \text{ mA}$$


This is the value for the equivalent Norton current source.

Example #6:

Find Z_n for the circuit in Figure 19–33 (Example 19–13) viewed from the open across terminals A and B .

Solution First, replace V_s with its internal impedance (zero), as indicated in Figure 19–35.

FIGURE 19–35

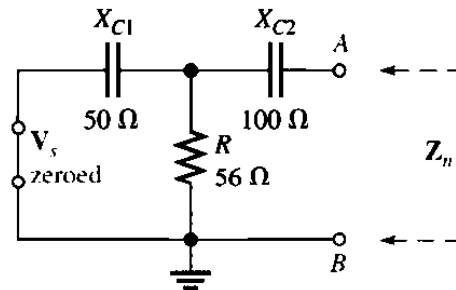

Looking in between terminals A and B , C_2 is in series with the parallel combination of R and C_1 . Thus,

$$\begin{aligned} Z_n &= X_{C2} + \frac{R X_{C1}}{R + X_{C1}} = 100 \angle -90^\circ \Omega + \frac{(56 \angle 0^\circ \Omega)(50 \angle -90^\circ \Omega)}{56 \Omega - j50 \Omega} \\ &= 100 \angle -90^\circ \Omega + 37.3 \angle -48.2^\circ \Omega \\ &= -j100 \Omega + 24.8 \Omega - j27.8 \Omega = 24.8 \Omega - j128 \Omega \end{aligned}$$

The Norton equivalent impedance is a 24.8Ω resistance in series with a 128Ω capacitive reactance.