



# ISRA UNIVERSITY

Islamabad Campus

Program: BTECH (Electrical)  
Semester – Spring 2018


ETCA-252 Circuit Analysis-II

Assignment – 3 **Solution**  
Marks: 15

**Due Date: 21/05/2018**  
**Handout Date: 14/05/2018**

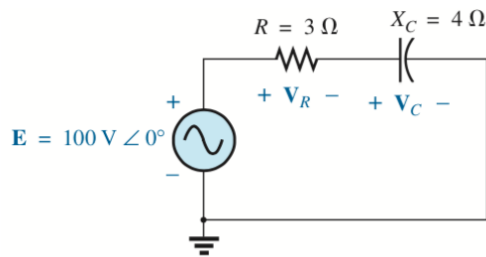Question # 1:

Using the voltage divider rule, find the voltage across each element of the circuit:




Solution:

$$\begin{aligned} V_C &= \frac{Z_C E}{Z_C + Z_R} = \frac{(4 \Omega \angle -90^\circ)(100 \text{ V } \angle 0^\circ)}{4 \Omega \angle -90^\circ + 3 \Omega \angle 0^\circ} = \frac{400 \angle -90^\circ}{3 - j4} \\ &= \frac{400 \angle -90^\circ}{5 \angle -53.13^\circ} = \mathbf{80 \text{ V } \angle -36.87^\circ} \\ V_R &= \frac{Z_R E}{Z_C + Z_R} = \frac{(3 \Omega \angle 0^\circ)(100 \text{ V } \angle 0^\circ)}{5 \Omega \angle -53.13^\circ} = \frac{300 \angle 0^\circ}{5 \angle -53.13^\circ} \\ &= \mathbf{60 \text{ V } \angle +53.13^\circ} \end{aligned}$$

---

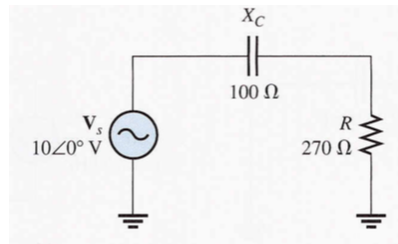Question # 2:

Express the total impedance of the following circuit in both polar and rectangular form:



Solution:

The impedance in rectangular form is:


$$\mathbf{Z} = R - jX_C = 270\Omega - j100\Omega$$

The impedance in polar form is:

$$\begin{aligned} \mathbf{Z} &= \sqrt{R^2 + X_C^2} \angle -\tan^{-1}\left(\frac{X_C}{R}\right) \\ &= \sqrt{(270\Omega)^2 + (100\Omega)^2} \angle -\tan^{-1}\left(\frac{100\Omega}{270\Omega}\right) = 287.9 \angle -20.32^\circ\Omega \end{aligned}$$

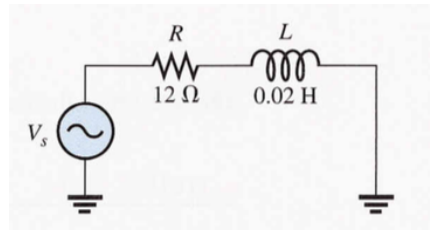Question # 3:

Determine the impedance at 1kHz, for the following circuit:



Solution:

The Inductance is as follows at 1kHz frequency:

$$X_L = 2\pi fL = 2\pi(1000\text{Hz})(0.02\text{H}) \Rightarrow 125.66\Omega$$

The impedance in rectangular form is:

$$\mathbf{Z} = R + jX_L = 12\Omega + j125.66\Omega$$

The impedance in polar form is:

$$\begin{aligned} \mathbf{Z} &= \sqrt{R^2 + X_L^2} \angle \tan^{-1}\left(\frac{X_L}{R}\right) \\ &= \sqrt{(12\Omega)^2 + (125.66\Omega)^2} \angle \tan^{-1}\left(\frac{125.66\Omega}{12\Omega}\right) = 127 \angle 84.5^\circ\Omega \end{aligned}$$

**Good Luck**