



# ISRA UNIVERSITY

Islamabad Campus

Program: BTECH (Electrical)  
Semester – Spring 2018

ETCA-252 Circuit Analysis-II

Assignment – 4 & 5  
Marks: 50

**Due Date: 19/06/2018**  
**Handout Date: 29/05/2018**

Question # 1:

Perform the following operations:

1.  $(8 + j5) + (2 + j1)$
2.  $(3 + j4) - (1 + j2)$
3. *Multiply:*  $(50\angle 10^\circ)(30\angle -60^\circ)$

**(Marks 06)**

Solution:

1.  $(8 + j5) + (2 + j1)$

$$(8 + j5) + (2 + j1) = (8 + 2) + j(5 + 1) \Rightarrow 10 + j6$$

2.  $(3 + j4) - (1 + j2)$

$$(3 + j4) - (1 + j2) = (3 - 1) + j(4 - 2) \Rightarrow 2 + j2$$

3. *Multiply:*  $(50\angle 10^\circ)(30\angle -60^\circ)$


$$(50\angle 10^\circ)(30\angle -60^\circ) = (50)(30)\angle(10^\circ + (-60^\circ)) \Rightarrow 1500\angle -50^\circ$$

---

Question # 2:

For the circuit in figure below, determine the following in polar form:

1.  $Z$
2.  $I_{\text{tot}}$
3.  $V_R$
4.  $V_C$

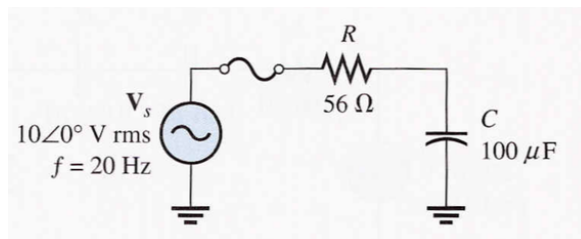

**(Marks 10)**

Solution:

$$X_C = \frac{1}{2\pi fC} = \frac{1}{2\pi(20\text{Hz})(100 \times 10^{-6})} \Rightarrow 79.6\Omega$$

1.  $Z$

$$\begin{aligned} Z &= \sqrt{R^2 + X_C^2} \angle -\tan^{-1}\left(\frac{X_C}{R}\right) \\ &= \sqrt{56\Omega^2 + (79.6\Omega)^2} \angle -\tan^{-1}\left(\frac{79.6\Omega}{56\Omega}\right) \Rightarrow 97.32 \angle -55^\circ\Omega \end{aligned}$$

2.  $I_{\text{tot}}$

$$\begin{aligned} I_{\text{tot}} &= \frac{V}{Z} = \frac{10 \angle 0^\circ}{97.32 \angle -55^\circ\Omega} \\ &= \frac{10}{97.32} \angle (0^\circ - (-55^\circ)) \Rightarrow 103 \angle 55^\circ \text{ mA} \end{aligned}$$

3.  $V_R$

$$\begin{aligned} V_R &= \left( \frac{R}{\sqrt{R^2 + X_C^2}} \right) V_{in} \angle \phi = \left( \frac{56\Omega}{97.32\Omega} \right) (10 \angle 55^\circ) \\ &\Rightarrow 5.76 \angle 55^\circ\Omega \end{aligned}$$


4.  $V_C$

$$\begin{aligned} V_C &= \left( \frac{X_C}{\sqrt{R^2 + X_C^2}} \right) V_{in} \angle \phi = \left( \frac{79.6\Omega}{97.32\Omega} \right) \left( 10 \angle -\tan^{-1}\left(\frac{R}{X_C}\right) \right) \\ &\Rightarrow 8.18 \angle -35.1^\circ\Omega \end{aligned}$$

---

Question # 3:

Determine the magnitude and phase angle of the total impedance:

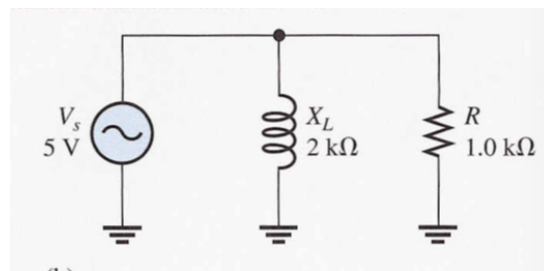

**(Marks 10)**

Solution:

The total impedance is:


$$\mathbf{Z} = \left( \frac{(1.0 \text{ k}\Omega)(2 \text{ k}\Omega)}{\sqrt{(1.0 \text{ k}\Omega)^2 + (2 \text{ k}\Omega)^2}} \right) \angle \tan^{-1} \left( \frac{1.0 \text{ k}\Omega}{2 \text{ k}\Omega} \right) = 894 \angle 26.6^\circ \Omega$$

Thus,  $\mathbf{Z} = 894 \Omega$  and  $\theta = 26.6^\circ$ .

The positive angle indicates that the voltage leads the current, as opposed to the RC case where voltage lags the current.

Question # 4:

Find the total current in the load resistor,  $R_L$ . Assume the sources are ideal.

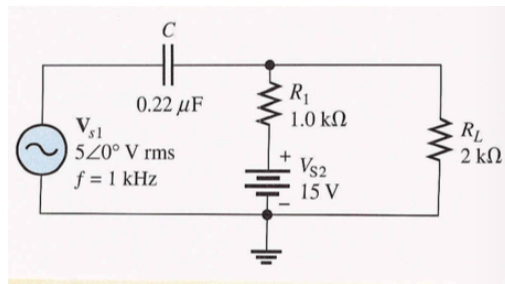

(Marks 10)

Solution:

**Step 1.** Find the current through  $R_L$  due to the ac source  $V_{s1}$  by zeroing (replacing with its internal impedance) the dc source  $V_{s2}$ , as shown in Figure 19–8. Looking from  $V_{s1}$ , the impedance is

$$\mathbf{Z} = \mathbf{X}_C + \frac{\mathbf{R}_1 \mathbf{R}_L}{\mathbf{R}_1 + \mathbf{R}_L}$$

$$\mathbf{X}_C = \frac{1}{2\pi(1.0 \text{ kHz})(0.22 \mu\text{F})} = 723 \Omega$$


$$\begin{aligned} \mathbf{Z} &= 723 \angle -90^\circ \Omega + \frac{(1.0 \angle 0^\circ \text{ k}\Omega)(2 \angle 0^\circ \text{ k}\Omega)}{3 \angle 0^\circ \text{ k}\Omega} \\ &= -j723 \Omega + 667 \Omega = 984 \angle -47.3^\circ \Omega \end{aligned}$$

The total current from the ac source is

$$\mathbf{I}_{s1} = \frac{\mathbf{V}_{s1}}{\mathbf{Z}} = \frac{5 \angle 0^\circ \text{ V}}{984 \angle -47.3^\circ \Omega} = 5.08 \angle 47.3^\circ \text{ mA}$$

Use the current-divider approach. The current in  $R_L$  due to  $V_{s1}$  is
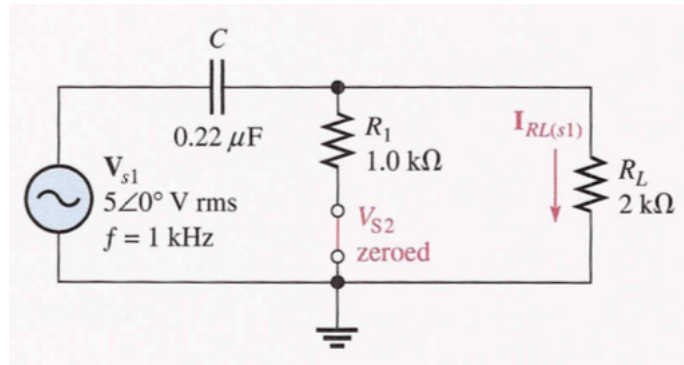
$$\mathbf{I}_{RL(s1)} = \left( \frac{R_1}{R_1 + R_L} \right) \mathbf{I}_{s1} = \left( \frac{1.0 \text{ k}\Omega}{3 \text{ k}\Omega} \right) 5.08 \angle 47.3^\circ \text{ mA} = 1.69 \angle 47.3^\circ \text{ mA}$$




**Step 2.** Find the current in  $R_L$  due to the dc source  $V_{S2}$  by zeroing  $V_{S1}$  (replacing with its internal impedance), as shown in Figure 19–9. The impedance magnitude as seen by  $V_{S2}$  is


$$Z = R_1 + R_L = 3 \text{ k}\Omega$$

The current produced by  $V_{S2}$  is
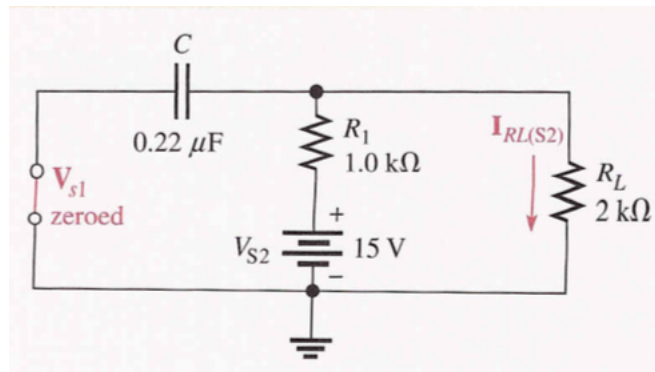
$$I_{RL(S2)} = \frac{V_{S2}}{Z} = \frac{15 \text{ V}}{3 \text{ k}\Omega} = 5 \text{ mA dc}$$




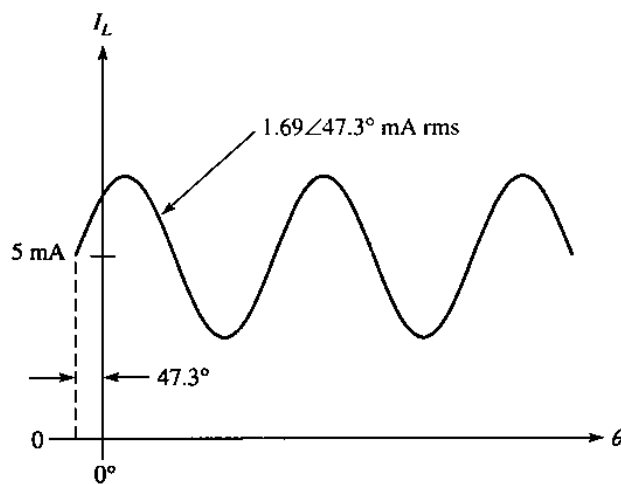**Step 3.** By superposition, the total current in  $R_L$  is  $1.69 \angle 47.3^\circ$  mA riding on a dc level of 5 mA, as indicated in Figure 19–10.



Question # 5:

Determine  $V_{th}$  and  $Z_{th}$  for the circuit within the beige box and draw its Thevenin Equivalent.

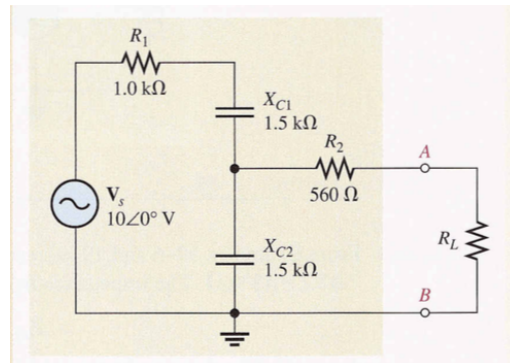

(Marks 10)


Solution:

Thevenin's voltage for the circuit between terminals  $A$  and  $B$  is the voltage that appears across  $A$  and  $B$  with  $R_L$  removed from the circuit.

There is no voltage drop across  $R_2$  because the open between terminals  $A$  and  $B$  prevents current through it. Thus,  $V_{AB}$  is the same as  $V_{C2}$  and can be found by the voltage-divider formula.

$$\begin{aligned} V_{AB} = V_{C2} &= \left( \frac{X_{C2} \angle -90^\circ}{R_1 - jX_{C1} - jX_{C2}} \right) V_s = \left( \frac{1.5 \angle -90^\circ \text{ k}\Omega}{1.0 \text{ k}\Omega - j3 \text{ k}\Omega} \right) 10 \angle 0^\circ \text{ V} \\ &= \left( \frac{1.5 \angle -90^\circ \text{ k}\Omega}{3.16 \angle -71.6^\circ \text{ k}\Omega} \right) 10 \angle 0^\circ \text{ V} = 4.75 \angle -18.4^\circ \text{ V} \\ V_{th} = V_{AB} &= \mathbf{4.75 \angle -18.4^\circ \text{ V}} \end{aligned}$$

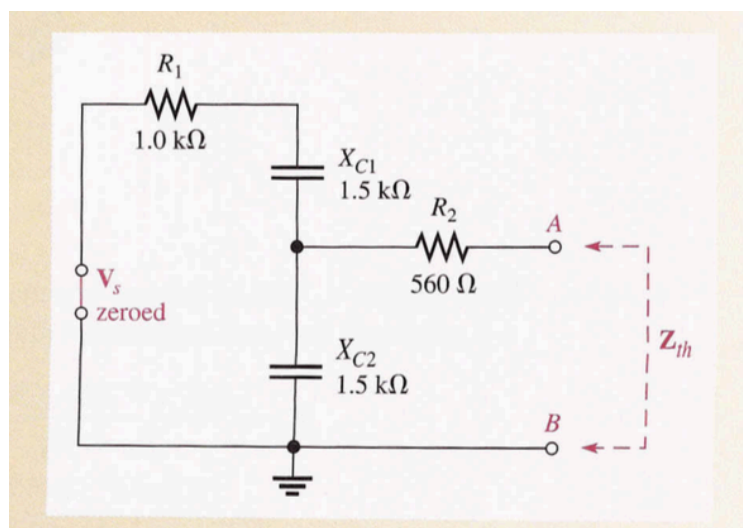For calculating  $Z_{th}$ , first replace the voltage source with its internal impedance (zero in this case) as shown below:




Looking from terminals  $A$  and  $B$ ,  $C_2$  appears in parallel with the series combination of  $R_1$  and  $C_1$ . This entire combination is in series with  $R_2$ . The calculation for  $Z_{th}$  is as follows:

$$\begin{aligned}
 Z_{th} &= R_2 \angle 0^\circ + \frac{(X_{C2} \angle -90^\circ)(R_1 - jX_{C1})}{R_1 - jX_{C1} - jX_{C2}} \\
 &= 560 \angle 0^\circ \Omega + \frac{(1.5 \angle -90^\circ \text{ k}\Omega)(1.0 \text{ k}\Omega - j1.5 \text{ k}\Omega)}{1.0 \text{ k}\Omega - j3 \text{ k}\Omega} \\
 &= 560 \angle 0^\circ \Omega + \frac{(1.5 \angle -90^\circ \text{ k}\Omega)(1.8 \angle -56.3^\circ \text{ k}\Omega)}{3.16 \angle -71.6^\circ \text{ k}\Omega} \\
 &= 560 \angle 0^\circ \Omega + 854 \angle -74.7^\circ \Omega = 560 \Omega + 225 \Omega - j824 \Omega \\
 &= 785 \Omega - j824 \Omega = 1138 \angle -46.4^\circ \Omega
 \end{aligned}$$

In rectangular form, the impedance is:


$$Z_{th} = 785\Omega - j824\Omega$$

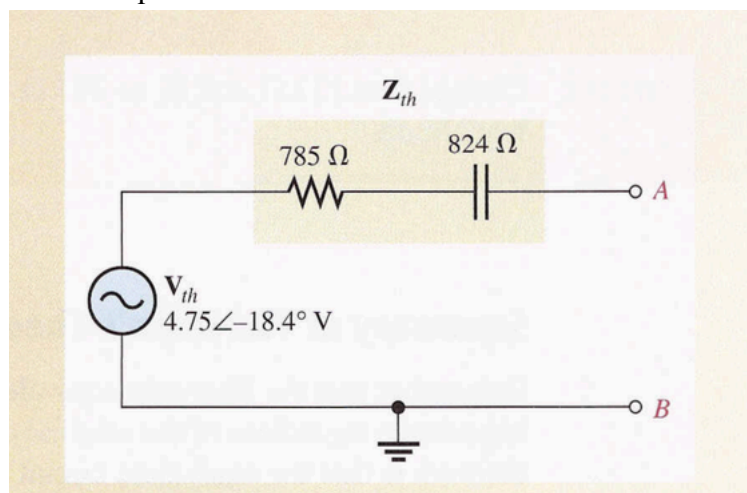The Thevenin equivalent circuit is as below:



Question # 6:


For a given circuit,  $I_n = 5\angle 0^\circ \text{ mA}$ , and  $Z_n = 150 \Omega + j100\Omega$ . Draw the Norton equivalent circuit.

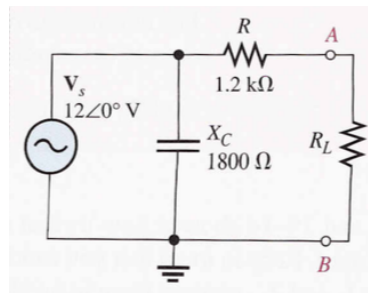

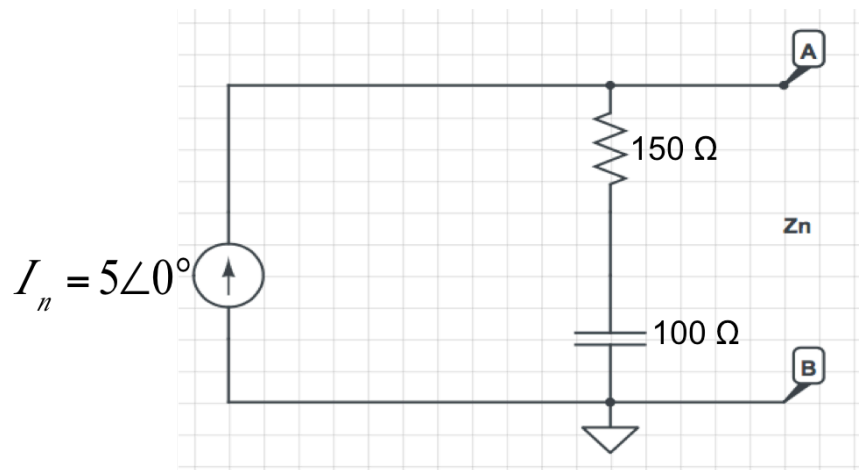**(Marks 04)**

Solution:

The Norton equivalent circuit is as follows:



---

**Good Luck**